

## GUJARAT TECHNOLOGICAL UNIVERSITY

B.E. Sem-III Remedial Examination May 2011

Subject code: 130901

Subject Name: Circuits and Networks

Date: 25-05-2011

Time: 10.30 am – 01.00 pm

Total Marks: 70

### Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Symbols and notations have conventional meaning unless stated.
4. Figures to the right indicate full marks.

**Q.1 (a)** Give the relation between energy (E) and power (P). Derive the equations for the energy stored in a capacitor (C) and an inductor (L) using  $P=VI$ . **07**

**(b)** Prove the maximum power transfer theorem for a practical voltage source ( $V_s, R_s$ ). What is the maximum power that can be delivered if  $V_s=20\text{ V}$  and  $R_s=1\text{ Ohm}$ ? **07**

**Q.2 (a)** Derive a tree of the graph of the network in Fig.1. Determine the node voltages  $V_1$  and  $V_2$ , using the mesh analysis. **07**

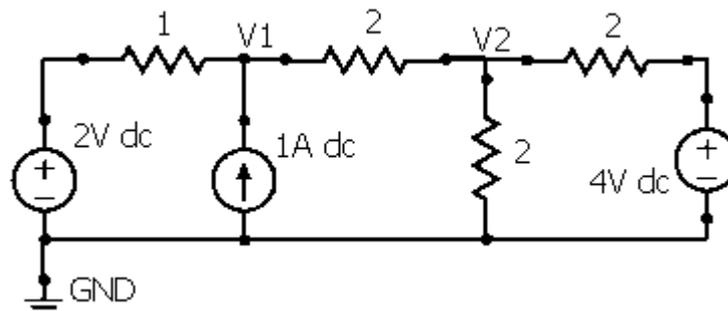


Figure 1 Network of Q. 2. Resistance values are in Ohms.

**(b)** Determine the node voltages  $V_1$  and  $V_2$  in the network shown in Fig. 1, by applying the superposition theorem. **07**

**OR**

**(b)** In Fig. 1, if 1 Ohm resistance is changed to 1.2 Ohm then determine the source-voltage for compensating for the change. **07**

**Q.3 (a)** Solve for the nodal voltages  $V_1, V_2, V_3$  and  $V_4$  as shown in the network in Fig. 2, using the nodal analysis. **07**

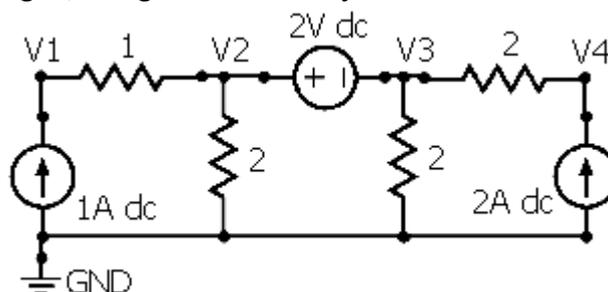


Figure 2 Network of Q. 3. Resistance values are in Ohms.

**(b)** In Fig. 2, if 2V source is replaced by an open circuit then find Thevenin's and Norton's equivalent circuits across  $V_2$  and  $V_3$ . **07**

**OR**

**Q.3 (a)** Find the equivalent inductance for the series and the parallel connections of L1 and L2 if their mutual inductance is M. **07**

**(b)** State Millman's theorem. Obtain the equivalent of a parallel connection of three branches each with a voltage source and a series resistance, (2V, 1 Ohm), (3V, 2 Ohm) and (5V, 2 Ohm). **07**

**Q.4 (a)** Define the time-constant of RL and RC networks and explain the significance of the time-constant. **07**

**(b)** Explain how to determine the initial conditions in an RL network and the current  $i(t)$  based on these conditions. **07**

**OR**

**Q.4 (a)** Obtain the loop-current  $i(t)$  in the RC network in Fig. 3, by solving the differential equation of the loop. **07**

**(b)** Obtain the voltage across the capacitor  $V_c(t)$ , in the LC circuit in Fig. 4 using Laplace transform technique if  $V_c(0)=2V$ . **07**

**Q.5 (a)** Determine the voltage across the capacitor in the RLC circuit as shown in Fig. 5, if  $R=400$  Ohm using Laplace transform. **07**

**(b)** Determine the poles of a series RLC circuit, if  $R=120$  Ohm,  $L=10$  mH and  $C=1$  micro-F. Sketch the pole-plot and comment on the nature of the response. **07**

**OR**

**Q.5 (a)** Explain the short-circuit admittance and the open-circuit impedance parameters for a two port network. **07**

**(b)** Draw a tree of the network in Fig. 6 taking the branches denoted by (b2), (b4), and (b5) as tree branches. Give the fundamental loop matrix. Determine the matrix loop equation from the fundamental loop matrix. **07**

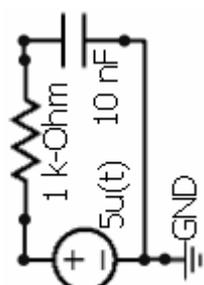


Figure 3 RC network of Q.4 (a).

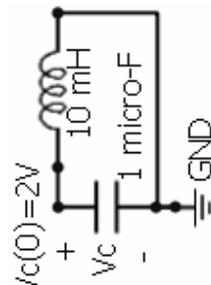


Figure 4 LC network of Q. 4 (b).

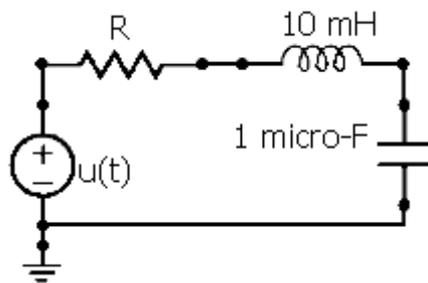


Figure 6 RLC circuit of Q. 5 (a).

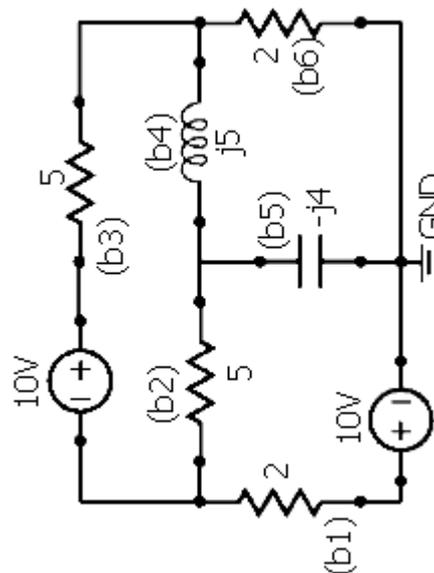


Figure 5 Network of Q. 5 (b). Branch-impedances are in Ohms.

\*\*\*\*\*