

**GUJARAT TECHNOLOGICAL UNIVERSITY**B.E. Sem-V<sup>th</sup> Examination December 2010

Subject code: 151006

Subject Name: Applied Electronics

Date: 21 /12 /2010

Time: 03.00 pm - 05.30 pm

Total Marks: 70

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

**Q.1 (a)** What is regulated power supply ? Draw and explain block diagram of SMPS. **07**  
Also write advantage of SMPS.

**(b)** Draw and explain the operational amplifier's closed loop configuration with necessary equation and compare all. **07**

**Q.2 (a)** Draw and explain block diagram of IC 555. Also explain the Pin connection of IC 555 **07**

**(b)** Design a astable multivibrator using IC 555 and draw its circuit diagram which generate output signal with frequency of 1kHz and duty cycle of 75%. **07**

**OR**

**(b)** Design monostable mutivibrator using IC 555 and draw the circuit diagram which gives output of pulse width of 10  $\mu$ s. What voltage must be applied to the CONTROL pin to stretch pulse width from

(i) 10  $\mu$ s to 20  $\mu$ s. (ii) 10  $\mu$ s to 5  $\mu$ s.

**Q.3 (a)** Give detail classification of the transducer and explain each of them in detail. **07**

**(b)** What is LVDT ? Explain principle and operation of LVDT. Also list the advantage and application of LVDT. **07**

**OR**

**Q.3 (a)** What is LCD? List the types of Liquid crystal and explain any two of them. **07**

**(b)** What is SCR? With required figure explain the operation and I-V characteristics of SCR. **07**

**Q.4 (a)** What is LASCR? Draw and explain construction and characteristics of LASCR in detail. **07**

**(b)** What is storage oscilloscope? Explain principle and working of storage oscilloscope. Also write the advantages and disadvantages of storage oscilloscope compare to CRO. **07**

**OR**

**Q.4 (a)** What is multimeter ? Draw and explain the block diagram of Digital Multimeter. Give comparison of analog and digital mutimeter. **07**

**(b)** With necessary figure, Explain block diagram, operation, and future of washing machine. **07**

**Q.5 (a)** What is universal Gate ? Explain NOR and NAND gate as a universal Gate. **07**

**(b)** Obtain minimal Sum Of Product for the function  $F(A,B,C,D,E) = \{0,2,4,6,9,11,13,15,17,,21,25,27,29,31\}$ . **07**

**OR**

**Q.5 (a)** Draw the block diagram of CD player and explain each blocks in detail. **07**

**(b)** Find out the Boolean expression of the Full Adder sum and carry. Using by same expression give realization of Full adder circuits. **07**

\*\*\*\*\*