

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEM-V Examination-Nov/Dec.-2011

Subject code: 150903

Date: 26/11/2011

Subject Name: Power Electronics-I

Time: 2.30 pm -5.00 pm

Total marks: 70

Instructions:

1. **Attempt all questions.**
2. **Make suitable assumptions wherever necessary.**
3. **Figures to the right indicate full marks.**

- Q.1 (a)** Draw the internal diagram of an SCR (specifying the different layers and their doping levels) and hence, explain the various operating modes of the device. Also draw the static V- I characteristic of the SCR **07**
- (b)** Describe the working of single phase fully controlled bridge converter connected to R – L load. Sketch the waveforms of (i) load voltage (ii) load current (iii) thyristor current and voltage for $\alpha = 45^\circ$ **07**
Hence derive the expression for rms load voltage.
- Q.2 (a)** For an SCR, the G –K characteristic is a straight line with a slope of 16 V/A passing through the origin. The maximum turn on time is 4 μ sec and the minimum gate current required for this quick turn on is 500 mA. If the gate source voltage is 15 V, calculate **07**
- i. The resistance to be inserted in the series with the SCR gate
 - ii. The gate power dissipation given that the pulse width is equal to the turn on time and average gate power dissipation is 0.3 W
 - iii. The maximum triggering frequency that will be possible when pulse triggering is used
- (b)** What do you understand by ‘commutation of SCR’. What are the conditions required for successful commutation. Hence explain Class C – Complementary Commutation method. **07**

OR

- (b)** Explain how UJT works as a relaxation oscillator. Hence, with neat diagram and waveforms, describe the line synchronized UJT triggering circuit. **07**
- Q.3 (a)** Explain the following current and voltage ratings of a thyristor **07**
- i. Peak working forward blocking voltage
 - ii. Peak repetitive reverse voltage
 - iii. Average on state current
 - iv. I^2t rating

- (b) What is the need of a snubber circuit. Discuss the function of each component and hence mention the steps involved in the design details (selecting the values) of each component when used in a d.c. circuit. 07

OR

- Q.3** (a) Compare MOSFET with SCR in terms of basic structure, V-I characteristics, ratings, control principle, applications etc. 07
- (b) With the help of appropriate waveforms and equations, show how the source inductance reduces the average output voltage of a single phase full converter. 07

- Q.4** (a) Write a note on single phase dual converter showing the circuit configuration and details of operation. What are the applications of such a dual converter? 07
- (b) Explain in brief various control strategies of a chopper 07

OR

- Q.4** (a) Explain the operation of a three phase, half controlled bridge converter with associated waveforms for $\alpha < 60^\circ$. Derive the expression for average output voltage. Will the average output voltage change for $\alpha > 60^\circ$? 07
- Q.4** (b) Draw the circuit configuration of step up chopper and explain its working. Derive its output voltage equation in terms of duty cycle and input voltage. 07

- Q.5** (a) Explain the operation of 1-phase fully controlled converter to operate a separately excited DC motor in 1st and 4th quadrant. Derive the expression for speed-torque characteristic of the DC motor and clearly mention how the characteristics will change with the change in firing angle. 07
- (b) Classify various chopper circuits based on principle of operation, circuit configuration etc. 07

OR

- Q.5** (a) Explain how a chopper circuit can be employed in the regenerative braking operation of a d.c. motor. Derive the expression for the range of speed control. 07
- (b) A d.c. chopper is used for regenerative braking of a separately excited dc motor. The dc supply voltage is 400 V. The motor has $R_A = 0.2 \Omega$ and $K_m = 1.2 \text{ V-s/rad}$. The average current during regenerative braking is constant at 300 A. For a duty cycle of 60% , determine
- Power returned to the dc supply
 - Minimum and maximum permissible braking speeds
 - Speed during regenerative braking
