

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE SEM-VII Examination-Nov/Dec.-2011**

**Subject code: 172401****Date: 19/11/2011****Subject Name: Power Electronics Systems Modelling****Time: 10.30 am-01.00 pm****Total marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and Explain the block diagram of Power Electronics System with reference to modeling. Explain feed-forward and disturbances w.r.t. to the block diagram in brief. **07**
- (b) State capacitor charge balance principle and explain its use in buck converter. **07**
- Q.2** (a) What do you mean by a normalized model? Explain in brief. Also explain the concept of controllability and observability in brief. **07**
- (b) Explain the manipulation of buck-boost converter model into canonical form. **07**
- OR**
- (b) Explain the modeling of pulse width modulator with necessary waveforms and equations. Also draw the pwm model including sampler. **07**
- Q.3** (a) Find out the steady state output voltage for a boost chopper using small-ripple approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio  $M(D)$  and draw its graph. **07**
- (b) Discuss the concept of nonlinearity and the importance of perturbation & linearization with respect to power electronics giving an example. **07**
- OR**
- Q.3** (a) For a given buck converter, if the input voltage is 50 V, Mark Space Ratio is 0.25, Switching frequency is 100 kHz and load resistance is 10  $\Omega$ , calculate the value of  $V_o$  and I. Also find out the value of C such that the peak output voltage ripple  $\Delta V$  is 5% of  $V_o$ . **07**
- (b) List the major steps of engineering design process. Explain each in brief. **07**
- Q.4** (a) Develop the state space model of a buck converter. Draw necessary figures. **07**
- (b) Define the following: Model, Controllability, Observability, MIMO, Normalization, Impulse Response, Linearization **07**
- OR**
- Q.4** (a) Discuss the development of Canonical Circuit Model based on physical arguments giving its importance. **07**
- (b) Develop the state space model of a boost converter along with necessary figures. **07**
- Q.5** (a) Develop the model of Armature controlled DC servo motor. **07**
- (b) Draw and explain the ideal and physical models of AC transformer. **07**
- OR**
- Q.5** (a) Explain the close loop speed control of DC motor using power electronics converter. **07**
- (b) Formulate the state space model of full bridge inverter with a physical transformer **07**

\*\*\*\*\*