Date: 05/06/2017

Total Marks: 70

07

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III (OLD) - EXAMINATION - SUMMER 2017

Subject Code: 131101

Subject Name: Basic Electronics

Time: 10:30 AM to 01:00 PM

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

| Q.1 | (a) | Explain energy band diagram of insulator, semiconductor and conductor. | 07 |
|-----|-------------|--|----|
| | (b) | Explain Intrinsic and Extrinsic semiconductors. | 07 |

- **Q.2** Explain i) Zener diode, ii) Photodiode. (a)
 - Explain the operation of a P-N junction diode in the forward biased condition and draw **(b)** 07 the forward characteristics.

OR

- (b) Write a short note on Tunnel diode. Explain the V-I characteristics of the Tunnel diode. 07
- Draw the circuit diagram of full wave bridge rectifier and draw its input and output **Q.3** (a) 07 waveforms. Also state the equation for D.C. load current.
 - Draw the block diagram of a regulated D.C. power supply and explain the function of 07 **(b)** each block in it with relevant waveforms.

OR

| Q.3 | (a) | Explain the different types of clipping circuit. Draw the necessary waveforms. | | |
|-----|------------|--|---|--|
| | (b) | Draw switching waveforms of diode and explain i) Storage Time (t_s) | | |
| | | ii) Transition Time (t_t) , iii) F | everse Recovery time (t _{rr}) | |

Q.4 List the three source of instability of collector current and define three stability factors. 07 (a) Explain i) The Early Effect ii) Avalanche Breakdown in Zener diode **(b)** 07

OR

- Draw Voltage divider bias circuit. How it stabilizes operating point? 0.4 **(a)** 07 07
 - State and prove Miller's theorem and its dual. **(b)**
- **Q.5** (a) Give constructional details of JFET and give its characteristics. Why FET is called 07 voltage control devices?
 - Give the point of difference between BJT and FET. Also explain FET as voltage 07 **(b)** variable resistor.

OR

- Compare different types of power amplifiers based on the following factors: 07 0.5 (a) i) Conduction angele ii) Position of Q Point iii) Efficiency iv) Distortion
 - In a fixed bias circuit using silicon npn transistor which has $\beta dc = 150$. The dc biasing **(b)** point is VCE = 5V & Ic = 5 mA, VCC = 10V. Find out value of Rb & Rc. 07


