## **GUJARAT TECHNOLOGICAL UNIVERSITY**

GUJAKAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-V (OLD) - EXAMINATION – SUMMER 2017				
Sı	ıbjec		Date: 15/05/2017	
Subject Name: Applied Electronics (Institute Elective - II)				
			Total Marks: 70	
In		ions: Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Enlist the characteristics of ideal op-amp. Classify Transducers.	07 07	
Q.2	(a) (b)	Enlist Application of 555 Timer circuits and explain one of them. What is Ideal Voltage source? Also explain factors affecting the voltage Regulation with block diagram of Shunt voltage regulator. <b>OR</b>	07 07	
	<b>(b)</b>	Explain (1) Load Regulation (2) Line Regulation	07	
Q.3	(a) (b)	Explain the working principle of SMPS. Write Short note on LED	07 07	
Q.3	(a) (b)	<b>OR</b> Enlist the types of closed loop configuration of an Op-amp and explain one of them. Write short note on Opto coupler.	07 07	
Q.4	(a) (b)	Explain SCR in Detail. Write Short note on CRO.	07 07	
Q.4	(a)	OR Explain UJT in Detail.	07	
Q.4	(a) (b)	Enlist Devices used in Consumer Electronics.	07 07	
Q.5	(a) (b)	Explain architecture of 8051 with block diagram. Explain fuzzy logic system to improve the performance of washing machine in detail.	07 07	
05	$(\mathbf{a})$	OR	07	
Q.5	(a) (b)	Explain Karnaugh map representation with example. Explain A/D convertor in detail.	07 07	

\*\*\*\*\*