Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

a		BE - SEMESTER-V (OLD) - EXAMINATION - SUMMER 2017	\ <b>-</b>
	•	et Code: 152402 Date: 05/05/20	)17
Ti	•	et Name: Electrical Measurements & Electronics Instruments 02:30 PM to 05:00 PM Total Marks:	70
111;	1. 2.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a)	State various types of errors in potential transformer. Explain how they can be reduced.	07
	<b>(b)</b>	Explain the classification of Electrical and Electronics Instruments.	07
Q.2	(a)	Explain principle and operation of PMMC instrument. Derive torque equation for it.	07
	<b>(b)</b>	Explain the calibration of voltmeter and ammeter using potentiometer. <b>OR</b>	07
	<b>(b)</b>	Define measurement. Draw the diagram of generalized measurement system. Explain the standards of measurement in detail.	07
Q.3	(a) (b)	Explain the Hay's bridge for measurement of inductance.  Explain the construction and working of D'Arsonval Galvanometer.  OR	07 07
Q.3	(a)	Explain the Kelvin double bridge method of measurement of low resistance in detail.	07
	<b>(b)</b>	Explain the Schering's bridge for measurement of capacitance.	07
Q.4	(a) (b)	Explain the static and dynamic characteristics of measuring instruments.  Explain the testing of instrument transformer.  OR	07 07
Q.4	(a)	With neat diagram explain construction and operation of single phase energy meter.	07
	<b>(b)</b>	Write short note on how to extend range of different instruments.	07
Q.5	(a)	Define Q-factor of Inductor. Explain the working of Digital LCR Meter with neat block diagram.	07
	<b>(b)</b>	Explain the op-amp voltage follower and op-amp amplifier type voltmeters. <b>OR</b>	07
Q.5	(a) (b)	Explain Maxwell's bridge with necessary diagrams.  Explain the construction and working of poly phase energy meter.	07 07

\*\*\*\*\*