Enrolment No.\_\_\_\_\_

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VI (OLD) - EXAMINATION - SUMMER 2017** 

Subject Code: 162404

Subject Name: Industrial Drives & Control - I

Time: 10:30 AM to 01:00 PM

## Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Discuss necessities of DC Drives. Draw and explain conventional block 07 diagram of various Drives.
  - (b) Explain the operation of 1-phase full converter with conventional current 07 condition having high speed & high inductive load for separately excited DC motor at  $\alpha = 30^{\circ}$ . Also draw various wave-forms.
- Q.2 (a) Explain the operation of single phase semi-converter circuit for DC Series 07 Motor with discontinuous armature current condition at  $\alpha = 45^{\circ}$ . Draw various wave forms.
  - (b) Derive the formula of speed and torque for DC Series motor for single phase 07 semi-converter and full-converter operation. Also draw the speed-torque characteristics.

OR

(b) Derive the equation of speed and torque for separately excited DC shunt motor for single phase full converter. Also draw speed – torque characteristics and control characteristics for the same.

| Q.3        | (a)        | Explain the operation of 3-phase full converter with conventional current condition for separately excited DC motor at $\alpha = 60^{\circ}$ . Also draw various wave- | 07 |
|------------|------------|--|----|
|            | (b)        | forms.<br>Discuss dual converters and its various field of applications.   | 07 |
|            | ()         | OR   | 01 |
| Q.3        | <b>(a)</b> | Discuss permanent magnet motor Drive.  | 07 |
| C          | <b>(b)</b> | Compare P, PI & PID controller.  | 07 |
| Q.4        | <b>(a)</b> | Draw and explain class A Chopper.  | 07 |
| C          | <b>(b)</b> | Derive the equation for average output voltage of boost chopper circuit.   | 07 |
|            |            | OR   |    |
| Q.4        | (a)        | Discuss importance of PI control for DC Drive.   | 07 |
| -          | <b>(b)</b> | Explain modelling of DC Motor controlled through armature voltage control.   | 07 |
| <b>Q.5</b> | (a)        | Discuss microcomputer control of DC Drive with the help of block diagram.  | 07 |
| ·          | (b)        | Explain multi-phase chopper circuit. Enumerate its merits & demerits.  | 07 |
|            | . /        | OR   |    |
| Q.5        | (a)        | Explain closed loop control of DC Drive.   | 07 |
| -          | (b)        | Explain Servo Motor Drive.   | 07 |

\*\*\*\*\*

Date: 03/05/2017

**Total Marks: 70**