Date: 09/05/2017

Total Marks: 70

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII (OLD) - EXAMINATION - SUMMER 2017

Subject Code: 170801

Subject Name: Power Electronics and Industrial Drives

Time: 02:30 PM to 05:00 PM

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Make a comparison of SCR, BJT,MOSFET and IGBT based on the following 07 parameters, 1) Power rating
 - 2) Switching speed
 - 3) Switching and conduction losses.
 - (b) Draw and explain the structure of power IGBT. Also explain principal of 07 operation and I-V characteristics of power IGBT.
- Q.2 (a) Explain 1-phase full bridge inverter with 90 degree mode of conduction. Draw 07 necessary Waveforms and equation.
 - (b) Briefly discuss the 180 degree operation of inverter circuit with appropriate 07 waveforms.

OR

- (b) Briefly discuss the 120 degree operation of inverter circuit with appropriate 07 waveforms.
- Q.3 (a) Briefly discuss the operation of on off controller (Integral Cycle Controller) 07 with neat sketch of its waveform.
 - (b) Briefly describe the operation of single phase cycloconverter with necessary 07 waveform.

OR

- Q.3 (a) Classify power factor improvement methods for phase controlled rectifiers.07 Explain Any one.
 - (b) Draw and explain single phase full wave controlled rectifier with the inductive 07 load using required waveforms and equations.
- Q.4(a) Discuss the class B operation of Chopper Circuit07(b) Explain control mode of DC-DC converter drives07

OR

- Q.4(a) Discuss about choice of AC and DC drive in detail07(b) Discuss the rotor voltage control for slip ring induction motor.07
- Q.5 (a) Comparison between voltage source inverter and current source inverter. 07
 - (b) Explain techniques of voltage control of single phase inverter. Explain single 07 pulse width Modulation.

OR

- Q.5 (a) Discuss the operation of 3 phase half wave controlled rectifier with R-L load. 07 Also Discuss the effect of free-wheeling diode in detail.
 - (b) Explain three phase cycloconverter and sinusoidal harmonic reduction 07 techniques for cycloconverter.
