GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII (OLD) - EXAMINATION - SUMMER 2017

BE - SEMESTER–VII (OLD) - EXAMINATION – SUMMER 2017			
Subject Code: 171002			Date: 02/05/2017
Subject Name: Power Electronics			
Time: 02:30 PM to 05:00 PM			Total Marks: 70
Instructions:			
	1.	1 1	
	2.	Make suitable assumptions wherever necessary.	
	3.	Figures to the right indicate full marks.	
Q.1	(a)	Describe two transistor model of Thyristor.	07
C	(b)	Explain principle of operation of pulse width modulated invert	er. 07
Q.2	(a)	Write short note on Switched mode Power Supply.	07
	(b)	List and describe Turn-on methods of Thyristor.	07
		OR	
	(b)	List and describe any two Turn-off methods of Thyristor.	07
Q.3	(a)	Write short note on single phase controlled rectifier.	07
	(b)	Explain principle of operation of step-up DC chopper.	07
		OR	
Q.3	(a)	Write short note on three phase controlled rectifier.	07
	(b)	Explain principle of operation of step-down DC chopper.	07
Q.4	(a)	Write short note on three phase inverter.	07
	(b)	Explain device structure and characteristics of IGBT.	07
		OR	
Q.4	(a)	Write short note on buck-boost converter.	07
	(b)	Write short note on RF heating.	07
Q.5	(a)	Write short note on performance parameters of inverter.	07
	(b)	Write short note on Battery charger.	07
OR			
Q.5	(a)	Write short note on single phase inverter.	07
	(b)	Write short note on Uninterruptible Power Supply.	07
