Enrolment No	Enrolment	No
--------------	-----------	----

Date: 04/05/2017

**Total Marks: 70** 

07

# **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VII (OLD) - EXAMINATION - SUMMER 2017** 

Subject Code: 172403

Subject Name: Power Processing Circuits - II

Time: 02:30 PM to 05:00 PM

## Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Explain basic series inverter circuit employing load commutation and also state 07 limitation of this series inverter.
  - (b) Discuss each component of UPS in brief.
- Q.2 (a) Explain the modified Mc-Murray half-bridge inverter with circuit diagram and 07 waveforms.
  - (b) Explain single phase 7 level asymmetric cascaded H bridge multilevel inverter 07 with circuit diagram and switching table.

#### OR

- (b) What are the advantages of multilevel inverter over conventional two-level **07** inverter?
- Q.3 (a) Explain active front-end rectifier with block diagram. What are the advantages 07 of active front-end rectifier over controlled rectifier?
  - (b) Describe the operation of a three phase bridge inverter for 180° conduction for 07 star connected resistive load.

OR

- Q.3 (a) Explain the space vector with its representation. Explain the space vector 07 sequence with waveforms.
  - (b) Explain phase dead-banding and draw the modulation reference waveforms for 07 it. Explain triplen injection modulation.
- Q.4 (a) Explain L type zero current switching resonant converter with circuit diagram 07 and waveforms.
  - (b) Explain the single-phase bidirectional controller having RL load with neat 07 waveforms.

#### OR

**Q.4** (a) Compare ZVS and ZCS.

- (b) Explain the operation of bridge type single-phase to single-phase cycloconverter 07 with continuous load current. Draw neat waveforms.
- Q.5 (a) Draw the block diagram of a typical battery charger and explain each block in 07 brief. Also explain the Ampere-Hour calculation for battery.
  - (b) Explain Integral Cycle Control method for AC voltage controllers.

### OR

- Q.5 (a) Explain the Fourier analysis of a square wave inverter and thus derive the THD 07 in the output voltage waveform.
  - (b) Explain the battery charging process and Ampere-Hour calculation for battery. 07

\*\*\*\*\*

07

07