Seat No.:	Enrolment No.

## GUJARAT TECHNOLOGICAL UNIVERSITY

C1	• <b>•</b> •••	BE - SEMESTER-VIII (OLD) - EXAMINATION – SUMMER 2017	
Sul Tin	ject	Code:180907 Date:06/05/2017 Name: Advanced Power Electronics II (Department Elective - II) 0:30 AM to 01:00 PM Total Marks: 70 ns:	)
	1. A 2. N	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a) (b)	What is FACTS? Discuss the advantages of FACTS in brief. State the types of HVDC systems and explain each in brief.	07 07
Q.2	<ul><li>(a)</li><li>(b)</li></ul>	Explain load compensation and system compensation with circuit and phasor diagram.  Explain the series compensation used for transmission line. & How it can useful to improve performance of system.	07 07
	<b>(b)</b>	OR  Explain the shunt compensation used for power system network. How it can be useful to improve the performance of system	07
Q.3	<ul><li>(a)</li><li>(b)</li></ul>	Explain working of TCR with circuit diagram & waveform. Derive the expression for susceptance of TCR.  Explain the working of TSC-TCR compensator with circuit & operating characteristic	07 07
Q.3	(a) (b)	OR Explain the characteristics of FC-TCR with and without coupling transformer. Compare technical performance of different SVCs.	07 07
Q.4	<ul><li>(a)</li><li>(b)</li></ul>	Explain the Operation of Three Phase Six Pulse controlled converter with equivalent circuit in each mode & waveform for delay angle.  Compare the classical HVDC and HVDC-VSC Systems  OR	07 07
Q.4	<ul><li>(a)</li><li>(b)</li></ul>	Draw the typical HVDC transmission scheme and explain the equipments required for HVDC system.  Compare EHV AC with HVDC transmission with reference to Economics of Transmission, Technical performance and Reliability. Draw relevant diagram	07 07
Q.5	(a) (b)	Derive the equation of PIV, peak to peak ripple and valve volt-ampere rating for a 6-pulse Graetz's converter circuit Discuss power reversal Characteristic of DC link and also Discuss Correction to inverter characteristics	07 07
Q.5	(a)	OR Explain the inverter operation of the 6-pulse converter with waveform.	07
V.S	(a) (b)	Explain Inverter Extinction Angle Control (EAG)	07