Seat No.:	Enrolment No.

## GUJARAT TECHNOLOGICAL UNIVERSITY

		BE - SEMESTER-VIII (OLD) - EXAMINATION – SUMMER 2017		
Subject Code:182401			Date:02/05/2017	
Ti	ime: 1 struct	et Name: Power Electronics Applications in Power System 10:30 AM to 01:00 PM Total Marks: ions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.	<b>7</b> 0	
Q.1	(a) (b)	Enlist various FACTS Controller & State advantages of each.  Explain basic block arrangement for interconnection of renewable energy sources to utility grid in brief.	07 07	
Q.2	(a) (b)	Discuss power quality standards. Explain IEEE 519 standard in brief. In accordance with HVDC converter define following terms (1) Firing Angle (2) Overlap Angle (3) Extinction Angle.  OR	07 07	
	<b>(b)</b>	Enlist & Explain various possible configuration of HVDC system.	07	
Q.3	(a) (b)	Draw & Explain 12 pulse AC-DC converter used in HVDC system.  Define THD. List and Explain need for improved utility interface.  OR	07 07	
Q.3	(a) (b)	Discuss Control of HVDC in brief.  Explain interface for a bidirectional power flow converter with necessary Diagrams.	07 07	
Q.4	(a) (b)	Explain the basic operating principle, characteristics and applications of STATCOM.	07 07	
0.4	( )	OR	0.5	
Q.4	(a) (b)	Explain the basic operating principle, characteristics and applications of SSSC. Explain Unified Power Flow Controller (UPFC) for Flexible AC Transmission.	07 07	
Q.5	(a)	Enumerate the advantages of static relays over electromagnetic relays. Also specify the limitations of static relays.	07	
	<b>(b)</b>	Discuss in brief : FC-TCR  OR	07	

\*\*\*\*\*

Q.5 (a) Explain directional static over current relay with neat block diagram.(b) Write a short note on TSC-TCR.

07 07