Seat No.:	Enrolment No.
Deat 110	Lin officit 110

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) - EXAMINATION - SUMMER 2017

Subject Code: 2130305 Date: 05/06/2017

Subject Name: Analog Circuits-I

Time: 10:30 AM to 01:00 PM Total Marks: 70

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1		Short Questions	14			
	1	Define positive feedback. elaborate its merits and demerits?				
	2					
	3	What is hall effect? State any one application. Why it is not possible to have infinite CMPP? Justify				
	4	Why it is not possible to have infinite CMRR? Justify.				
	5	Define Total output offset voltage. What is multivibrator?				
	6	What is meant by voltage-comparator?				
	7	Draw the output waveforms of Astable multivibrator?				
	8	Draw the circuit of Schmitt trigger?				
	9	Why is the bridge not used to give phase shift?				
	10	What disadvantages does a phase shift oscillator have?				
	11	Which are two types of impurities? State their examples.				
	12	What is doping and dopant? Why doping is necessary?				
	13	Explain the formation of n type of semiconductor.				
	14	What is Unity-Gain Bandwidth?				
Q.2	(a)	Explain the characteristics of an Ideal Op-amp. Mention	03			
		two applications of Op-Amp.				
	(b)	With neat circuit diagram and waveforms, explain the				
		working of a half wave rectifier.				
	(c)	With a neat circuit diagram, explain the Voltage Divider	07			
		Bias circuit using approximate analysis.				
		OR				
	(c)	Give points of difference between BJT and FET. Also	07			
0.2	(0)	explain FET as voltage variable resistor.	02			
Q.3	(a)	Give the difference between inverting and non-inverting Op-amp.	03			
	(b)	Draw common emitter circuit and sketch the input and	04			
		output characteristics. Also explain operating regions by				
		indicating them on characteristics curve.				
	(c)	Describe briefly the construction and working of p	07			
		channel enhancement MOSFET. Draw its characteristic				
		and transfer curve.				
0.2	(0)	OR Write different types of D. N. innetions. Explain formation	02			
Q.3	(a)	Write different types of P-N junctions. Explain formation of P N junction begring potential in P N junction	03			
	(b)	of P-N junction, barrier potential in P-N junction.	04			
	(0)	Derive the relationship between α and β . Calculate the	U 7			
		value of I_c , I_e for a transistor that has $\alpha = 0.98$ and $I_b = 100 \mu A$.				

MARKS

	(c)	Give constructional details of JFET and give its	07
		characteristics. Why FET is called voltage controlled	
		device?	
Q.4	(a)	Explain about slew rate & its effects. Derive the expression	03
•	` /	for slew rate.	
	(b)	Write short note on Antilog Amplifier.	04
	(c)	Explain with diagrams the principle of operation & design	07
	(-)	of an Astable multivibrator using 555 timers.	
		OR	
Q.4	(a)	Draw the circuit diagram of voltage follower. What are its	03
	()	closed loop voltage gain and bandwidth?	
	(b)	What is Window Detector? What is the use of Window	04
	()	Detector?	
	(c)	Draw & explain the circuit of a RC phase shift Oscillator.	07
	(-)	Derive an expression for its frequency of operation.	
Q.5	(a)	Write short note on Differentiator using OP-AMP.	03
	(b)	Explain BJT as a switch.	04
	(c)	Explain instrumentation Amplifier & derive its expression	07
	(-)	for output voltage.	
		OR	
Q.5	(a)	Draw the circuit diagram of differential amplifier with a	03
	()	gain of 10 and write the expression for the output voltage.	
	(b)	Explain the effect of temperature on a p-n junction diode.	04
	(c)	Write Short notes on: Clipper and Clampers	07
	(-)	II F	0.
