GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-III (NEW) - EXAMINATION - SUMMER 2017

Subject Code: 2130306 Date: 09/06/2017

Subject Name: Fundamentals of Digital Design

Time: 10:30 AM to 01:00 PM Total Marks: 70

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Marks 14

Q.1 Short Questions

- 1 A+A.B =
 - **A** A
- **B** AB
- **C** 1+B
- **D** 1

2 The truth table of 5 input NOR gate will have _____ rows to include all possible input combination.

- **A** 12
- **B** 64
- **C** 16
- **D** 32

3 Adding inverters to the input of an OR gate produces logic function.

- A NOR
- B NAND
- C AND
- **D** Ex-OR

4 A 6 variable K map for SOP form has ____cells.

- **A** 6
- **B** 16
- **C** 32
- **D** 64

5 If two voltage levels are -5 and -10, in negative logic the -5v level is called level.

- $\mathbf{A} \quad 0$
- **B** 1
- **C** 0.5
- **D** All

6 number of flip-flops are required to reduce frequency by 32.

- **A** 3
- **B** 4
- **C** 6
- **D** 5

7 A ring counter uses FFs.

- \mathbf{A} D
- **B** JK
- C RS
- \mathbf{D} T

8 The output for a gate is low when at least one input is low, the gate is

- A AND
- **B** OR
- C NAND
- **D** NOR

9 The output for a gate is high if and only if all inputs are low, the gate is

- A Ex-OR
- **B** NAND
- C NOR
- \mathbf{D} OR

10 Draw the truth table of Ex-OR and Ex-NOR Gates.

- 11 What is the full form of FPGA?
- 12 Define SSI, MSI, LSI and VLSI.
- 13 Give difference between combinational and sequential circuits.

14 List different types of logic family of integrated circuits.

Q.2	(a)	The product of maxterm form of the function xy+x'z is						03
	(b)	Simplified $\sum (0,1,2,3,4,5,6)$	Boolean 5,12,13,14,15).	function	of	function	F(A,B,C,D)=	04
	(c)	Design a combinational circuit of full adder.						
		OR						
	(c)	Design a combinational circuit of full substractor.						
Q.3	(a)	Convert hexa decimal number (ABCD) ₁₆ into decimal, binary and octal number.						
	(b)	Subtract two binary numbers using 2's complement: 1101-1110 =						
	(c)	Simplified Boolean function of $F(A,B,C,D,E) = \sum (0,2,4,6,9,11,13,15,17,21,25,29,31) + d(1,5).$						
		OR						
Q.3	(a)							
	(b)	using Boolean algebra. Simplify Boolean function $f(A,B,C,D) = \pi(0,1,2,3,4,5,6,12,13,14,15)$ using K-						
	(b)	Simplify Boolean function f (A,B,C,D) = $\pi(0,1,2,3,4,5,6,12,13,14,15)$ using K-MAP.						
	(c)	Simplified Boolean function of						
	(-)	$F(A,B,C,D,E) = \sum (0,2,4,6,9,11,13,15,17,21,25,29,31)$ using tabulation method.						
Q.4	(a)	Draw and expl	ain encoder.					03
	(b)							
	(c)	Draw and explain 4 bit magnitude comparator circuit OR						
Q.4	(a)	Write a short n	ote on multipl	_				03
	(b)	<u> </u>						04
	(c)	Draw and expl	ain BCD adde	r circuit.				07
Q.5	(a)	Draw and explain JK flip flop.						03
	(b)	Write a short n						04 07
	(c)							
<u> </u>	, .	OR Draw and explain T flip flop.						
Q.5	(a)	1 1 1						
	(b)	1 1 1						04
	(c)	Explain different types of ADC.						07
