Seat No.:	Enrolment No.

**Subject Name: Circuits and Networks** 

What is potential difference?

2. Make suitable assumptions wherever necessary.

3. Figures to the right indicate full marks.

Time: 10:30 AM to 01:00 PM

Do as directed:

1. Attempt all questions.

70

**Q.1** 

**Instructions:** 

1

(c)

(a)

(c)

**Q.3** 

**Q.4** 

represented by

the figure -6.

for the load  $R_I$ .

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

BE - SEMESTER-III (NEW) - EXAMINATION – SUMMER 2017 Subject Code: 2130901 Date: 31/05/2017

**Total Marks:** 

14

Explain Ideal Voltage source. 2 Super position theorem is applicable to \_\_\_\_\_\_ and \_\_\_\_\_ network. 3 4 Justify: The inductors act as an open circuit at time  $t = 0_+$ . 5 State and explain: Principle of conservation of charge. 6 What is transfer function? Define: Poles and Zeros of network transfer function. 7 8 Define: Driving point impedance. 9 What is two-port network? 10 What is the condition for reciprocal network for h-parameters? 11 Define: Oriented Graph. 12 What is Tree and Co-tree? 13 Define: Tie-set. 14 Define: Incidence matrix. State and explain maximum power transfer theorem. Derive the condition for **Q.2** 03 maximum power transfer to load for DC circuit. Using the specified currents, write the Kirchhoff voltage law equations for the **(b)** 04 network given in figure -1. For the circuit of figure – 2, suppose  $V_{in} = 1 V$ . Find R so that  $V_{out}/V_{in} = 150$ . **07** (c) For the circuit of figure -3, using mesh analysis find the mesh currents  $I_1$ ,  $I_2$ 07 and  $I_3$ . Also fine voltage v across a dependent source. Q.3 (a) What is an impulse function? Find the impulse response h(t) for the network 03 function  $H(s) = 1/s^2 + 4s + 4$ . For the network shown in the figure – 4, determine  $G_{12} = V_2/V_1$ . 04 **(b)** 

For the network of the figure -5, show that the equivalent Thevenin network is

 $V_T = \frac{V_1}{2}(1 + p + q - pq)$  and  $R_T = \frac{3 - q}{2}$ 

Obtain the pole-zero plot of the transform impedance of the network shown in

For the network of the figure – 7, determine the Thevenin equivalent network

The network shown in the figure -8 is in the steady state with the switch K

The network shown in the figure -9 is in the steady state with the switch K

Determine the Laplace transform of  $f(t) = e^{-at} \cos \omega t$ .

open. At t = 0, the switch is closed. Determine the current i(t).

State and explain initial value theorem.

07

03

04

**07** 


03


04


closed. At t=0, the switch is opened. Determine the voltage across the switch,  $v_k$  and  $dv_k/dt$  at  $t=0_+$ .


OR

- Q.4 (a) Write the initial conditions in the inductor and capacitor at t = 0<sub>+</sub> and t = ∞.
  (b) In the network of the figure 10, the switch K is in position a for a long time.
  At t = 0, the switch is moved from a to b. Find v<sub>2</sub>(t) with assumption that the initial current in the 2 h inductor is zero.
  - (c) The network shown in the figure 11 is in the steady state with the switch K open. At t = 0, the switch is closed. Determine the values of  $v_a(0_-)$  and  $v_a(0_+)$ .
- Q.5 (a) Determine h-parameters in terms of z-parameters.
  - (b) For the resistive network shown in the figure -12, draw the oriented graph and tree. Also develop the fundamental tie-set matrix  $(B_f)$ .
  - (c) For the network shown in the figure 13, determine the y-parameters. 07
- Q.5 (a) Derive the condition for the network to be reciprocal for ABCD-parameters. 03
  - (b) For the resistive network shown in the figure -12, Develop the incidence -04 matrix A.
  - (c) For the network shown in the figure 13, determine the z-parameters. 07

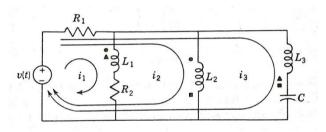

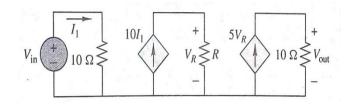

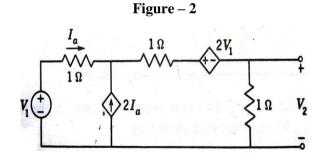

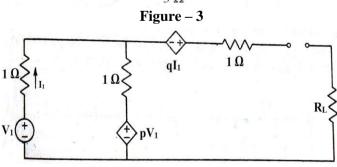

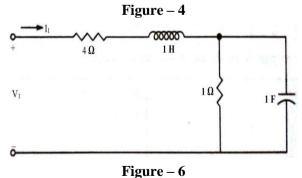


Figure – 5

