## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-IV (NEW) - EXAMINATION - SUMMER 2017** 

Subject Code: 2141002

Subject Name: Analog Circuit Design

Time: 10:30 AM to 01:00 PM

**Total Marks: 70** 

MARKS

14

03

Date: 30/05/2017

**Instructions:** 

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1 **Short Questions** 

- 1 Explain the behavior of transistor at high frequency.
- 2 Which Amplifier is often used to drive capacitive loads.
- 3 What is the suitable frequency range for wein bridge oscillator?
- 4 What is differential amplifier? How it is different from conventional amplifier?
- 5 Which type of negative feedback is present in inverting configuration?
- 6 Explain procedure of offset-nulling in op-amp.
- Explain any one application of I-V converter in brief. 7
- 8 How op-amp is used as a summing amplifier?
- Enlist the applications of comparator and explain PLD. 9
- What is multivibretor? Classify different multivibretors. 10
- Define and explain the 'Lock range' and 'Capture range'. 11
- 12 What is the difference between shunt and series regulator?
- 13 Explain the necessaity of high order filters.
- 14 What is the difference between active and passive filters?
- Explain Barkhausen criterion for oscillation in brief. Q.2 (a)
  - Design RC phase oscillator for the frequency of 2 KHz. 04 **(b)**
  - Draw op-amp based wein bridge oscillator. Obtain frequency of 07 (c) oscillation and discuss amplitude stabilization for same.

## OR


- Derive the expression for the frequency for the RC phase shift oscillator (c) 07 using transistor.
- Q.3 A Hartley oscillator circuit has a tank circuit inductance of 03 **(a)**  $L_1=L_2=100\mu$ H. It is required to produce oscillations at 50 KHz. Obtain the exact value of the tank circuit capacitance for the above requirement. 04
  - State the relation between hybrid- $\Pi$  and h-parameters. **(b)**
  - Draw and explain with necessary figure the single stage CE amplifier (c) 07 response. Also explain the significance of GB product.

## OR

- Q.3 Derive the necessary equation of gain for All pass filter. 03 **(a)** 
  - Design on Op-Amp Schmitt trigger with LTP = 2V, UTP = 4V and **(b)** 04 Vsat= $\pm 10$  V.
  - Draw circuit diagram of differential amplifier with three op-amps and (c) 07 derive expression for its output signal as a function of input signals.
- Define PSRR of an op-amp. If PSRR of an op-amp is 150µv/v and **Q.4** 03 **(a)** supply voltage changes from +10v to +12v, what is the change in V<sub>i0</sub>.
  - An op-amp as inverting amplifier is driven by 10 V peak to peak sine **(b)** 04

wave. Supply voltage of op-amp is +/- 15V. Draw input and output waveforms and give your comments.

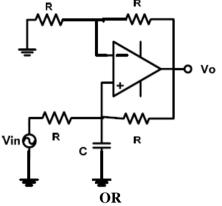(c) Prove that output is integral function of Input.



- Q.4 (a) Define the following. (i) CMRR (ii) Slew Rate (iii) Offset voltage. 03
  - (b) Draw and explain working of op-amp based Full wave rectifier circuit.
  - (c) Explain voltage to current converter with floating load. Based on that 07 show low voltage DC voltmeter circuit and discuss it.
- Q.5 (a) Discuss fixed and adjustable voltage regulator with necessary circuit 03 diagrams.
  - (b) For an astable multivibretor using 555 timer,  $R_A=4.7K\Omega$ ,  $R_B=1K\Omega$  and  $C=0.05\mu$ F, determine the positive pulse width, negative pulse width and free running frequency.
  - (c) Design and explain the  $2^{nd}$  order low pass butterworth filter. Derive the equation of gain for the same. 07

## OR

- **Q.5** (a) Calculate output frequency fo, lock range and and capture range of a **03** PLL if  $R_T=1K\Omega$ ,  $C_T=0.1\mu F$  and filter capacitor C=10  $\mu F$  and V=20v.
  - (b) Explain the magnitude and phase response of low pass function of 04 biquad circuit.
  - (c) Explain with the circuit diagram and waveforms, the monostable 07 multivibretor using 555 timer. Design the same for output pulse width of 10ms.

\*\*\*\*\*

07

04