Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (NEW) - EXAMINATION - SUMMER 2017

Subject Code: 2142405 Date: 01/06/2017

Subject Name: Analog Electronics and Its Applications

Time: 10:30 AM to 01:00 PM **Total Marks: 70**

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

MARKS 0.1 **Short Ouestions** 14 1 Rectification Efficiency of HW Diode Rectifier with R Load is %. 2 Ripple Factor of FW Diode Rectifier with R Load is _____. 3 PIV for Diode Bridge Rectifier is _____ volts. CE Configuration of BJT is commonly used because ------4 AC / DC Load lines decides ______ in amplifier. 5 Voltage Regulated IC 7812 is used for _____ volts. Full Form of CMRR is ______& PSRR is _____. 7 8 Zero Crossing Detector circuit is one type of ______. NIC & FDNR are types of -----. 9 Oscillator Circuit needs input(s). **10** IC-555 is invariably used in applications such as -----. 12 Logic Gates belongs to ______ scale Integrated Circuit. 13 Slew Rate is the measurement of in Op-amp. 14 Filter Circuits block the ----- component & pass ----- component. 03 0.2 (a) Compare Diode with Bipolar Junction Transistor. Give comparative statements in Tabular form for CE, CB, CC 04 Configuration of BJT. **07** Draw and explain Full Wave Rectifier circuit diagram and various waveforms having capacitor filter for R – Load. OR (c) Draw and explain Full Wave Rectifier circuit diagram and various **07** waveforms without capacitor filter for RL-Load. 0.3 (a) Draw Class-C amplifier circuit and specify its applications. 03 (b) Draw Class - A amplifier circuit and specify its applications and 04 limitations. Explain 78xx and 79xx voltage regulators. Draw necessary circuit **07** diagram to get 12-volt constant output using 7812 IC. (a) Discuss Ideal Op-amp. 03 0.3 **(b)** Discuss practical Op-amp Characteristics. 04 Draw the basic block diagram, symbol, characteristics and equivalent **07** circuit of Operational Amplifier. List the type and important parameters of Op-amp. 03 Draw Peak Sample and Hold Circuit using Op-amp. **Q.4**

	(b)	Draw and explain Precision Rectifier Detector using Op-amp.	
	(c)	Explain clipper and clamper circuits using Op-amp with necessary diagram & waveforms. Give applications of it.	07
		OR	
Q.4	(a)	Discuss Phase Shift Oscillator.	03
	(b)	Discuss Wien Bridge Oscillator.	04
	(c)	Draw and explain the circuit diagram and various waveforms for Triangular Wave Generator.	07
Q.5	(a)	Discuss MF5 switched Capacitor Filter.	03
	(b)	Draw block diagram of V/F converter and explain its working.	04
	(c)	Explain bistable multivibrator using 555. Give necessary equations and draw neat diagram and waveforms.	07
		OR	
Q.5	(a)	Enlist the possible name of logic gates. Enumerate the advantages of logic	
		gates.	
	(b)	Construct and explain a logic gate using Discrete Components.	04
	(c)	Give possible comparative statements for DTL, TTL & RTL in tabular forms.	07
