Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-IV (NEW) - EXAMINATION - SUMMER 2017

Subject Code: 2142406 Date: 06/06/2017

Subject Name: Digital Electronics and its applications

Time: 10:30 AM to 01:00 PM Total Marks: 70

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.

Q.1		Short Questions	14
	1	$(153)_{10} = ()_8$	
	2	What is role of complements in Digital Computer?	
	3	Define Register.	
	4	Give package name of Integrated circuits.	
	5	Draw block diagram of combinational circuit?	
	6	Multiplexer is circuit. (Sequential,	
		Combinational, Counter, Analog).	
	7	Draw block diagram of PLA.	
	8	1 Kilobyte = () bytes.	
	9	Draw symbol of buffer and Inverter.	
	10	Define FLIP-FLOP.	
	11	What is volatile memory? Give its types.	
	12	• • • • • • • • • • • • • • • • • • • •	
	13	Draw block diagram of ROM.	
	14	<u> </u>	
Q.2	(a)		03
		examples.	
	(b)	State and prove De 'Morgan's Theorems with the help of truth	04
		tables.	
	(c)	Simplify the Boolean function using K-MAP.	07
		$F = \Sigma(0,1,2,4,5,6,8,9,12,13,14).$	
		OR	
	(c)	Explain with necessary diagram AND-OR-INVERT and	07
		OR- AND-INVERT Implementation.	
Q.3	(a)		03
		be overcome.	
	(b)	Compare Combinational logic and Sequential logic in tabular	04
	(a)	form.	07
	(c)	Write a brief note on edge-triggered SR and JK Flip-Flops.	07
Q.3	(a)	OR Explain how JK flip flop can be used to implement D flip flop.	03
Ų.J	(a) (b)	Construct 4×16 Decoder with help of two 3×8 Decoder.	03
	(c)	With logic diagram explain the operation of 4 bit binary ripple	07
	(0)	counter. How up counter can be converted into down counter?	07
Q.4	(a)	Explain the Concept of register transfer level.	03
~··	(b)	Explain with necessary sketches PLA control.	04
	(c)	What is tabulation method? Simplify the Boolean function	07
	` /	$F(w,x,v,z) = \Sigma(1.3.7.11.15)$ and don't care condition	

OR

Q.4	(a)	What is basic requirements of memory? Explain in brief	03
		EEPROM.	
	(b)	Explain in details Triggering of flip-flops.	04
	(c)	What do you understand by subtractor? Design a full-adder with	07
		two half-adders and an OR gate.	
Q.5	(a)	Compare RAM and ROM in all aspects.	03
	(b)	Discuss in brief micro-programmed control unit.	04
	(c)	Write a detailed note on: - Magnetic-core memory.	07
		OR	
Q.5	(a)	Compare SDRAM and DRAM in tabular form.	03
_	(b)	Define (1) Accumulator (2) ALU register	04
	(c)	Describe Processor organization using scratchpad memory with	07
		block diagram. What is the limitation of this type of organization	
		and how we overcome this Limitation?	
