

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V (NEW) - EXAMINATION – SUMMER 2017

Subject Code: 2152407

Date: 27/04/2017

Subject Name: Power Electronic Circuits-I

Time: 02:30 PM to 05:00 PM

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

| | | MARKS |
|------------|--|-----------|
| Q.1 | Discuss following in brief (One Mark Each) | 14 |
| | 1 Draw only symbol of SCR. | |
| | 2 Enlist various operating modes of Power BJT. | |
| | 3 Define Latching Current in SCR. | |
| | 4 Draw only Vertical Structure of IGBT. | |
| | 5 What is the importance of snubber circuit? | |
| | 6 List out different triggering methods of SCR. | |
| | 7 Draw only Planner Structure of MOSFET. | |
| | 8 Draw only Reverse Recovery Characteristics of Power Diode. | |
| | 9 Draw only V-I Characteristics of IGBT. | |
| | 10 Enlist various applications of DIAC. | |
| | 11 State various requirements of Driver Circuits for Power Semiconductor devices? | |
| | 12 Draw only symbol of GTO. | |
| | 13 What is a freewheeling diode, and what is its purpose? | |
| | 14 Draw the static V-I characteristic of TRIAC. | |
| Q.2 | (a) Draw connection diagram for transformer connections used in 24 Pulse Rectifier. | 03 |
| | (b) Discuss Star – Delta transformer connection used in multi-pulse Rectifier in detail. | 04 |
| | (c) Discuss the working of 1-Phase Dual Converter; also derive equation for necessary condition for operation of Dual converter. | 07 |
| | OR | |
| | (c) Explain operation of 1-Phase Half controlled rectifier with RL Load. Derive Equation for V_o (avg). | 07 |
| Q.3 | (a) Give brief discussion on Four Quadrant Chopper Circuit. | 03 |
| | (b) Compare 1-Phase Rectifier with 3-Phase Rectifier circuit. | 04 |
| | (c) Discuss operation of 3-Phase full wave controlled rectifier with R Load & $\alpha = 30^\circ$. | 07 |
| | OR | |
| Q.3 | (a) Draw circuit diagram of Jones Chopper. | 03 |
| | (b) Derive only equation for average o/p voltage of Full wave controlled rectifier with RL Load in continuous conduction mode. | 04 |
| | (c) Draw & explain operation of 1-Phase full wave controlled rectifier with RLE Load. | 07 |

- Q.4** (a) Enlist requirements of DC Power Supply. **03**
 (b) Derive only equation for Inductor used in Boost Converter. **04**
 (c) Discuss the working principle of resonant converters. State its classification and advantages. **07**
- OR**
- Q.4** (a) Draw only circuit diagram & waveforms for Buck-Boost converter. **03**
 (b) Derive equation for o/p voltage & critical value of Inductor in Buck-Boost converter. **04**
 (c) Write a Short note on M-type ZCS Resonant converter. **07**
- Q.5** (a) State advantages of Isolated DC-DC Converters. **03**
 (b) Explain only working of Fly-back converter with necessary diagrams. **04**
 (c) Write a short note on Half Bridge DC-DC Converter. **07**
- OR**
- Q.5** (a) Compare Half Bridge & Full Bridge Isolated DC-DC Converter. **03**
 (b) Discuss SEPIC Converter in Brief. **04**
 (c) Write a short note on Push-Pull type DC-DC Converter. **07**
