Enrolment No._____

CULLDAT TECHNOLOCICAL UNIVERSITY

		GUJARAT TECHNOLOGICAL UNIVERSITY	
Subje		BE - SEMESTER–VI (NEW) - EXAMINATION – SUMMER 2017 de: 2161709 Date: 05/0	5/2017
U		me: Programmable Logic Controller	5/201/
-		0 AM to 01:00 PM Total Ma	rke. 70
Instruct			1K5. /U
		npt all questions.	
2.	Mak	e suitable assumptions wherever necessary.	
		res to the right indicate full marks.	
4.	Assu	me necessary inputs and outputs if required	
			MARKS
Q.1		Short Questions	14
Q.1	1	What is full name of PLC?	14
	2	List out the disadvantages of PLC?	
	3	What is reliability?	
	4	Compare PLC with Microcontroller.	
	5	What is meaning of sink module?	
	6	What do the abbreviations NO and NC represent when used to	
		describe switch contacts?	
	7	What is the main advantage of the jump instruction?	
	8	Why are PLCs installed within an enclosure?	
	9	How does the inductive proximity sensor work?	
	10	How is PLC flexible?	
	11	List four I/O modules?	
	12	What is opto-coupler?	
	13	How do contactors differ from relays? What is "Run Mode" in PLC?	
0.2	14 (a)	Draw the block diagram of PLC.	03
Q.2	(a) (b)	List four factors that enter into the length of the scan time and	03 04
	(0)	explain it.	04
	(c)	Express the following equation in ladder logic program:	07
		1. 4 to 1 line multiplexer	
		2. F (a,b,c) = Σ (2,4,6,7)	
		OR	
	(c)	Write a PLC ladder logic equivalent for NAND and NOR as universal	07
0.2	(-)	gates.	02
Q.3	(a)	List preventive maintenance tasks that should be carried out on the PLC installation regularly.	03
	(b)	List eight different types of data files use by an SLC 500 controller.	04
	(c) (c)	Design a PLC program and prepare a typical I/O connection diagram	07
	(-)	and ladder logic program for the following motor control	
		specifications:	
		• Three starters are to be wired so that each starter is operated	
		from its own start/stop pushbutton station.	
		• A master stop station is to be included that will trip out all	
		starters when pushed.	
		• Overload relay contacts are to be programmed so that an	
		overload on any one of the starters will automatically drop all of	

the starters.

Q.3			
	(a)	Describe the Input Module block diagram.	03
	(b)	Explain the various programming languages in PLC	04
	(c)	A pump is to be used to fill two storage tanks. The pump is manually	07
		started by the operator from a start/stop station. When the first tank is	
		full, the control logic must be able to automatically stop flow to the	
		first tank and direct flow to the second tank through the use of	
		sensors and electric solenoid valves. When the second tank is full, the pump must shut down automatically. Indicator lamps are to be	
		included to signal when each tank is full.	
		1. Draw a sketch of the process.	
		2. Prepare a typical PLC program for this control process.	
Q.4	(a)	Name five pieces of information usually associated with a PLC timer	03
		instruction.	
	(b)	Explain the ON-Delay timer.	04
	(c)	Two feeder conveyors (F1 and F2) feed a part onto one main	07
		conveyor (M). A proximity device is at the end of each feeder	
		conveyor. The proximity device outputs are fed as pulses to counters.	
		Each counter then shows the count of parts being put onto the main	
		conveyor. In addition, another proximity device at the end of the	
		conveyor in response to parts leaving and then sends the pulses to	
		another counter. Develop a ladder program to have a single register showing the number counter of parts on the conveyor. Assume that	
		the register is initially set the same count as the count of parts on	
		conveyor.	
		OR	
Q.4	(a)	Name the three forms of PLC counter instructions, and explain the	03
		basic operation of each.	
	(b)	Set up a PLC program to obtain an output, P, in register OR0055.	~ 4
	()		04
	()	The output is to give a value based on two inputs, M and N. P equals	04
		the square of M plus the square root of N.	
	(c)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to	04 07
		the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to	
		the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write	
05	(c)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process.	07
Q.5		the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE	
Q.5	(c)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process.	07
Q.5	(c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL	07 03
Q.5	(c) (a) (b)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog	07 03 04
Q.5	(c) (a) (b)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts.	07 03 04
-	(c) (a) (b) (c)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR	07 03 04 07
Q.5 Q.5	(c) (a) (b) (c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC	07 03 04 07 03
-	(c) (a) (b) (c)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain:	07 03 04 07
-	(c) (a) (b) (c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain: 1. Byte to integer conversion	07 03 04 07 03
-	(c) (a) (b) (c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain: 1. Byte to integer conversion 2. ENI	07 03 04 07 03
-	(c) (a) (b) (c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain: 1. Byte to integer conversion 2. ENI 3. Bit Operation: RS and SR	07 03 04 07 03
-	(c) (a) (b) (c) (a) (b)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain: 1. Byte to integer conversion 2. ENI 3. Bit Operation: RS and SR 4. Read RTC	07 03 04 07 03
-	(c) (a) (b) (c) (a)	the square of M plus the square root of N. When the lights are turned off in a building, an exit door light is to remain on for an additional 2 min, and the parking lot lights are to remain on for an additional 3 min after the door light goes out. Write a ladder program to implement this process. Describe various move instructions: BIT, BYTE, WORD DOUBLE WORD, REAL Explain the PID control in PLC. Two liner input signals of 0 to 5 volts are to be multiplied and the result put out on a linear output of 0 to 10 volts using analog modules. Trace the number if the inputs are 2.85 and 3.45 volts. OR Describe the networking in PLC Explain: 1. Byte to integer conversion 2. ENI 3. Bit Operation: RS and SR	07 03 04 07 03 04
