## CULLDAT TECHNOLOCICAL UNIVED CITY

GUJARAT TECHNOLOGICAL UNIVERSITY			
<b>BE - SEMESTER-VII (NEW) - EXAMINATION - SUMMER 2017</b>			
Subject Code: 2170808 Date: 04/05/2017			
Subject Name: Sensor Networks & Instrumentation			
	Time: 02.30 PM to 05.00 PMTotal Marks:		
Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks.			
Q.1	<b>(a)</b>	What is Sensor? Give classification of sensors with respect to various parameters.	07
	<b>(b)</b>	Explain Thermal & Capacitive sensors in detail.	07
Q.2	<b>(a)</b>	How to select a sensor? Explain selection of sensor in detail.	07
	<b>(b)</b>	Explain Block Diagram & Ideal characteristics of Op-Amp.	07
	(b)	<b>OR</b> What is Negative Feedback? What are its advantages? Derive expression of negative feedback of Op-Amp in Inverting mode.	07
Q.3	(a)	Explain V-I and I-V converters using Op-Amp.	07
	(b)	Explain CO <sub>2</sub> sensor with neat block diagram, working and applications in detail. <b>OR</b>	07
Q.3	<b>(a)</b>	Explain Instrumentation Amplifier in detail using Op-Amp.	07
	<b>(b)</b>	Explain Trasnducer Bridge Amplifier using Op-Amp with Application.	07
Q.4	<b>(a)</b>	Explain applications of WSN in detail with suitable examples.	07
	<b>(b)</b>	Explain various factors influencing WSN design. OR	07
Q.4	(a)	Explain KRC filters and derive its equations.	07
<b>x</b>	(b)	Explain first order Low Pass active filter and derive its equation.	07
Q.5	<b>(a)</b>	Derive equation of second order high pass active filter with its advantages and limitations.	07
	<b>(b</b> )	Explain first order High pass passive filter in detail. OR	07
Q.5	(a)	Explain Zigbee Network in detail.	07
	(b)	Explain Multiple Feedback filters.	07

\*\*\*\*\*