

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-III • EXAMINATION – SUMMER 2013****Subject Code: 130701****Date: 27-05-2013****Subject Name: Digital Logic Design****Time: 02.30 pm - 05.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Convert the decimal number 250.5 to base 3, base 4, base 7 and base 16. **07**
 (b) Perform the subtraction with the following decimal numbers using 1's complement and 2's complements. (a) 11010-1101, (b) 10010-10011 **07**
- Q.2** (a) Simplify the following Boolean functions to a minimum number of literals. **07**
 (a) $xyz + x\bar{y} + xyz\bar{y}$ and (b) $(A+B)(A\bar{y} + B\bar{y})$
 (b) Obtain the truth table of the function $F = xy + xy\bar{z} + y\bar{z}$ **07**
- OR**
- (b) Implement the Boolean functions. **07**
- Q.3** (a) Implement the Boolean functions. (a) $xyz + x\bar{y} + xyz\bar{y}$ (b) $(A+B)(A\bar{y} + B\bar{y})$ and (c) $F = xy + xy\bar{z} + y\bar{z}$ with logic gates. **07**
 (b) Show that the dual of the exclusive-OR is equal to its complement. **07**
- OR**
- Q.3** (a) Obtain the simplified expression in sum of product for the following Boolean functions. (a) $F = \sum(0,1,4,5,10,11,12,14)$ and (b) $F = \sum(11,12,13,14,15)$. **07**
 (b) Implement the functions $F = \sum(1,3,7,11,15)$ with don't care conditions $d = \sum(0,2,5)$. Discuss the effect of don't care conditions. **07**
- Q.4** (a) Explain half and full adders in detail. **07**
 (b) Design and implement BCD to excess 3 code converter. **07**
- OR**
- Q.4** (a) What is the difference between serial and parallel transfer? What type of registers are used in each case? **07**
 (b) Design a synchronous BCD counter with JK flip flops. **07**
- Q.5** (a) Explain a 4 to 1 line multiplexer in detail. **07**
 (b) Explain PLA in detail. **07**
- OR**
- Q.5** (a) Explain scratchpad memory in detail. **07**
 (b) Explain D type positive edge triggered flip flop. **07**
