GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III • EXAMINATION – SUMMER 2013

Subject Code: 130901 Subject Name: Circuits and Networks Time: 02.30 pm - 05.00 pm Instructions:

Date: 04-06-2013

Total Marks: 70

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- Q.1 (a) Define following terms:
 - (1) Linear and Nonlinear networks (2) Lumped and Distributed networks
 - (3) Passive and Active networks (4) Dependent source
 - (b) For magnetically coupled network shown in Fig.-1, find dot-convention and

Write the KVL equations.


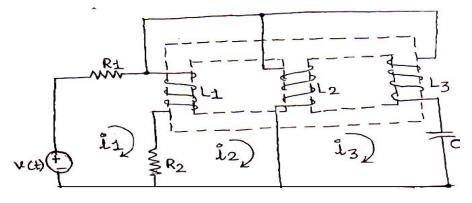


Fig.-1

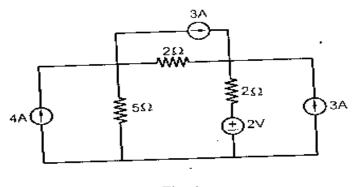Q.2 (a) Find currents through the resistors in the network of Fig.-2 using mesh analysis. 07






(b) Determine the current through 2 resistor of Fig.3 using source transformation. 07


07

07

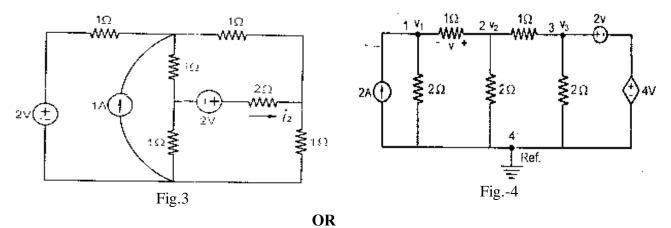

(b) In the network of Fig.-4 , determine the node voltages V_1 , V_2 and V_3 using node analysis.

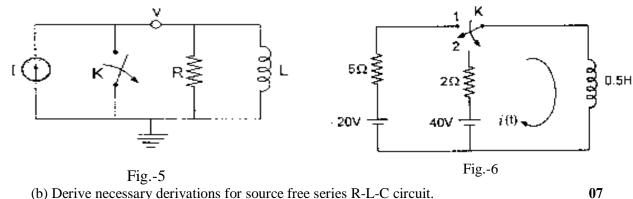
(a) In the network of Fig.-5 the switch K is opened at t=0. Find the values of V, dV/dtQ.3 and d^2V/dt^2 at t=0+ if I=10A, R=10 and L=1H. 07



(b) Derive necessary derivations for source free series R-L-C circuit.

OR

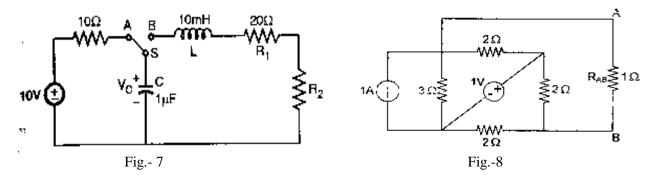(a) In the network of Fig.-6, the switch K is moved from 1 to 2 position at t=0, steady Q.3 07 state having previously been attained. Determine the current i(t). (b) In the network of Fig.-7, if the switch has remained in position A for a long time and then moves to position B at t=0. Find and plot Vc(t) for $t \times 0$ for R_2 = 405 . 07



(a) State and explain Nortonøs theorem. Q.4

07

(b) Discuss Duality in detail.

OR

- Q.4 (a) Determine the current in 1 resistor of the network of Fig.-8 using Theveninøs theorem.
 (b) Derive relationship between Z-parameters and Y-parameters. Discuss Reciprocity and symmetry of network in brief.
- Q.5 (a) In the network of Fig.-9, the switch K is moved from position a to b at t=0 (Steady state existing). Solve for the current i(t) using Laplace transformation method. 07

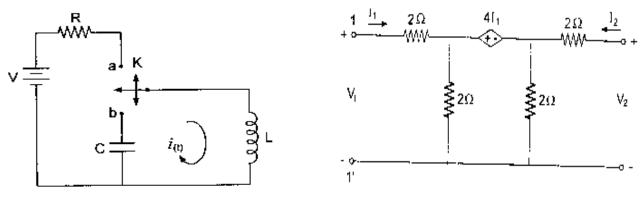


Fig.-9

Fig.-10

(b) Find Z-parameters for the network of Fig.- 10 .

OR

Q.5 (a) Explain the concept of poles and zeros and their significance.
(b) Define Sub-graph. For the circuit shown in Fig.-11, draw the graph and write the

(i) incidence matrix and (ii) cutset matrix.

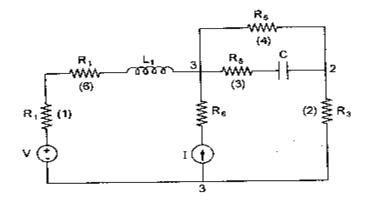


Fig.-11

07

07

07