GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-III • EXAMINATION – SUMMER 2013

Subject Code: 130902Date: 27-05-2Subject Name: Analog and Digital ElectronicsTotal MarksTime: 02.30 pm - 05.00 pmTotal MarksInstructions:Total Marks			27-05-2013	
)	
	1. A 2. M	ttempt all questions. Iake suitable assumptions wherever necessary. igures to the right indicate full marks.		
Q.1	(a) (b)	Explain OP-AMP as a comparator. State and explain De Morganøs theorem.	07 07	
Q.2	(a) (b)	Write short note on D flip flop. Define any seven OP-AMP parameters. OR	07 07	
	(b)	Explain Direct coupled and RC coupled amplifiers with its frequency response.	07	
Q.3	(a)	Write short note on integrator.	07	
	(b)	Describe astable multivibrator based on IC 555 and OP-AMP. OR	07	
Q.3	(a)	Draw and explain basic block schematic of 78XX series three terminal voltage regulator ICs.	07	
	(b)	Explain binary addition, subtraction, division and multiplication with example.	07	
Q.4	(a)	Write short note on gray code.	07	
-	(b)	Explain NOR gate as a universal gate. OR	07	
Q.4	(a)	Define any seven performance characteristics of digital ICs.	07	
Q.4	(b)	Write down truth tables for BCD to seven segment decoder for common anode and common cathode display.	07	
Q.5	(a)	Write short note on half adder and full adder.	07	
	(b)	Explain S-R flip flop.	07	
05	(-)	OR Write down modes of execution of shift register. Excloir any and sof	07	
Q.5	(a)	Write down modes of operation of shift register. Explain any one mode of operation in detail.	07	
	(b)	What is the basic difference between synchronous and asynchronous counter? Explain four bit synchronous up counter.	07	
