Seat No.:	Enrolment No.
Deat 110	Emoment 10

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V • EXAMINATION – SUMMER 2013

\mathbf{S}^{1}	ubje	ct Code: 150901 Date: 14-05-2013	
\mathbf{S}	ubje	ct Name: Electrical Machine - II	
	•	: 10.30 am - 01.00 pm Total Marks: 70	
		tions:	
		1. Attempt all questions.	
		2. Make suitable assumptions wherever necessary.	
		3. Figures to the right indicate full marks.	
Q.1	(a)		07
	(1)	Dz6 connection of 3-phase transformer.	~ =
	(b)		07
Q.2	(a)	converting 3-phase supply into two 1-phase supply using two 1-phase transformer With the help of a neat diagram explain parallel operation of two 3-phase	07
	(a)	transformers. Also explain the essential & desirable conditions to be fulfilled for	U/
		operating two 3-transformers in parallel.	
	(b)	Two transformers are connected in open delta and supply a balance 3-phase load of	07
		240 KW at 400 volt and a power factor of 0.866, determine	
		(1) The secondary line current, (2) The KVA load on each transformer,	
		(3) The power delivered by the individual transformers.	
	<i>a</i> >	OR	0=
	(b)		07
Q.3	(a)	Yz11 connection of 3-phase transformer. Draw the circle diagram for a 3-phase,6-pole,50hz,400 V star connected induction	10
Ų.J	(a)	motor from the following data	10
		No load test: 400V, 9A, 1250 watt; Short circuit test: 200V, 50A, 6930 watt	
		The stator loss at standstill is 55% of total copper losses and full load current is 32	
		A. determine (1) power factor, slip, output, efficiency, speed and torque at full load	
		(2) starting torque	
	(b)	Explain the phenomenon of cogging and crawling in induction motor.	4
0.2	(-)	OR	07
Q.3	(a) (b)	State and explain different speed control methods of 3-phase induction motor Explain principle and operation of 3-phase induction generator. Also state its	07 07
	(0)	application.	U/
Q.4	(a)	Explain double revolving field theory related to 1-phase induction motor. From this	07
	()	theory verify that 1-phase induction motor is not self started.	
	(b)	A 230V, 380W, 50Hz, 4-pole, 1-phase induction motor gave the following test	07
		results.	
		No load test: 230 V, 84 W, 2.8 A; Blocked rotor test: 110 V,460W, 6.2A	
		The stator winding resistance is 4.6 ohm and during the blocked rotor test the	
		auxiliary winding is open. Determine the equivalent circuit parameters. OR	
Q.4	(a)	Explain operation and principle of universal motor	07
Ţ.Ţ	(b)	Explain different methods of producing starting torque in 1-phase induction motor	07
Q.5	(a)	Explain construction and working principle of Schrage motor.	07
``	(b)	Explain the working, equivalent circuit and advantages of double squirrel cage	07
		induction motor.	
		OR	. –
Q.5	(a)	Explain construction and working principle of shaded pole induction motor.	07
	(b)	Explain construction of welding transformer. How does it differ from power	07
		transformer?	
