## **GUJARAT TECHNOLOGICAL UNIVERSITY** BE - SEMESTER-V • EXAMINATION – SUMMER 2013

Subject Code: 151003

## Date: 16-05-2013

# Subject Name: Integrated Circuits and Applications

## Time: 10.30 am - 01.00 pm

## **Total Marks: 70**

- Instructions:
  - 1. Attempt all questions.
  - 2. Make suitable assumptions wherever necessary.
  - 3. Figures to the right indicate full marks.
- Q.1 (a) 1. Draw block diagram of a typical op-amp and explain functions of each 04 block.
  - Define followings for an op-amp: (i) input offset current (ii) CMRR (iii) 03 Differential input resistance.
  - (b) What type of feedback is present in the non-inverting amplifier? Derive 07 expression for voltage gain, input resistance, output resistance and bandwidth of a non-inverting amplifier using a non ideal op-amp.
- Q.2 (a) 1. Draw inverting amplifier. Determine the maximum output offset voltage 04 due to (i) input offset voltage Vio and (ii) input bias current I<sub>B</sub>. Take Vio max = 6 mV dc, I<sub>B</sub> max = 500 A dc, Vs =  $\pm$  15 V, R<sub>F</sub> = 47 ká and R<sub>1</sub> = 470 á.
  - 2. What is slew rate? List causes of slew rate. Also explain its significance 03 in applications.
  - (b) Draw peaking amplifier specify the value of all components to provide a 07 gain of 10 at a peak frequency of 16 KHz. Take L = 10 mH with internal resistance of 30 á .

#### OR

- (b) What is an instrumentation amplifier? Explain with the help of neat 07 diagram the operation of an instrumentation amplifier employing three basic op-amps and with provision for variation in the voltage gain.
- Q.3 (a) Draw the non-inverting Schmitt trigger comparator circuit and explain the 07 threshold levels and hysteresis.
  - (b) Draw asymmetrical square-wave generator circuit using op-amp. Specify 07 suitable component value for the following specification:  $T_{ON} = 1$  sec.  $T_{OFF} = 2$  sec. Assume value of  $\beta = 0.1$  and  $C = 100 \ \mu F$ .

## OR

- Q.3 (a) Explain in detail operation of full-wave precision rectifier with neat 07 diagram and waveform.
  - (b) Draw basic log amplifier using a transistor. Derive the expression for 07 output voltage. Also state disadvantages of circuit.
- Q.4 (a) Design second order Butterworth low pass filter with 6 3 dB 07 frequency of 10 KHz. Choose C = 1 F. (Use equal component KRC filter circuit)
  - (b) With the help of a circuit diagram explain the operation of first order high- 07 pass filter.

- Q.4 (a) Design a wide-band band pass filter using a single op-amp for  $f_L = 100$  Hz, 07  $f_H = 1$  KHz and pass band gain of 4. Also calculate the value its quality factor Q.
- Q.4 (b) Derive the expression for filter transfer function of a first order low-pass 07 filter and draw its frequency response characteristics.
- Q.5 (a) Design a free running ramp generator using IC 555 for Vcc=10 V, C= 07  $0.1\mu$ F and period T= 2 ms. Take transistor with  $\beta = 100$ . Explain its working.
  - (b) Draw block diagram of the PLL system and explain function of each block. 07 State the applications of PLL.

#### OR

- Q.5 (a) Draw circuit diagram of an astable multivibrator using IC 555 and explain 07 its operation. Derive expression for frequency of operation and duty cycle.
  - (b) Draw block diagram of a basic SMPS and explain it. Also state advantages 07 and disadvantages of SMPS.

\*\*\*\*\*