Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V • EXAMINATION – SUMMER 2013

Date: 14-05-2013

Subject Code: 152401

Tiı	-	Name: Power Electronics Devices and Components 10.30 am - 01.00 pm Total Marks: 70 ons:	
	2.	Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	
Q.1	(a)	Draw the Block Diagram of Power Electronics System and Explain functionality and working of each block in detail.	07
	(b)	Explain V-I Characteristics of SCR and Derive equation of I _A using two transistor analogy of SCR.	07
Q.2	(a)	Design a Relaxation Oscillator using UJT for the triggering of SCR. The data is as follows. $\eta = 0.72$, $I_p = 0.6 mA$, $V_v = 1 V$, $I_v = 2.5 mA$, $V_{BB} = 18 V$, $R_{BB} = 5 k\Omega$, Leakage current with open emitter = 4.2 mA. The firing frequency is 2 KHz. For $C = 0.04 \mu F$, compute necessary resistances used in circuit.	07
	(b)	Define SOA. Explain FBSOA and RBSOA of Power BJT.	07
	(b)		07
Q.3	(a)	Define commutation. List different methods of commutation. Explain Class-D	07
	(b)	commutation with necessary circuit and waveforms List the causes of the voltage transient in thyristor. Suggest Protection circuit to ensure protection against high dv/dt and explain its working with neat sketch. OR	07
Q.3	(a)	Define Turn-On time of Thyristor. List different methods of Triggering. Explain R-C Triggering circuit with necessary circuit and waveforms.	07
	(b)	List the different losses occurring in Thyristor. Explain the Thermal Resistance. Explain importance of Heat Sink.	07
Q.4	(a) (b)	Explain four mode operation of TRIAC. Compare: 1. Schottky Diode and PIN Diode. 2. Power BJT and Power MOSFET. OR	07 07
Q. 4	(a) (b)	Explain the construction and V- I characteristics of MCT. Explain construction, working, transfer and output characteristics of N-Channel Enhancement Type MOSFET.	07 07
Q.5	(a) (b)	Write a Short Note on Materials used in Power Semiconductor Devices. Explain the construction and V- I characteristics of IGBT. OR	07 07
Q.5	(a) (b)	Write a Short Note on Power Integrated Circuit. What is Gate Drive? Explain gate drive for IGBT.	07 07
