Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

BE - SEMESTER-V • EXAMINATION – SUMMER 2013

U		ode: 152403 Date: 21-05-2013	
Subject Name: Applied Power Electronics Time: 10.30 am - 01.00 pm Instructions:		30 am - 01.00 pm Total Marks: 70	
Histru	1. A 2. M 3. I	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.  Notations / symbols used have usual meaning.	
Q.1	(a) (b)	What is PLL? Explain working principle of PLL with neat diagram.  Define Phase control. With help of block diagram, describe working of a controlled rectifier.	07 07
Q.2	(a)	What is Power Processing? What are different functions of it? What is its importance in Power Electronics?	07
	(b)	•	07
		OR	
	(b)	Draw detailed filter frequency response for: high-pass, low-pass, band-stop filter. How cut-off frequency is decided?	07
Q.3	(a) (b)	Explain the concept of HVDC transmission.  Explain working of following circuits with neat schematic diagram.	07 07
		(1) Log Amplifier (2) Peak detector.  OR	
<b>Q.3</b>	(a)	Write technical note on: Active power filter.	07
	(b)	Draw schematic diagram and working of switch capacitor filter. State its application.	07
Q.4	(a)	Explain SMPS with necessary schematic diagram.	07
•	(b)	State characteristics of Ultrasonic. Explain ultrasonic flow detector.  OR	07
Q.4	(a)	Describe basic principle of die-electric heating. Also, discuss the effect of parameter variation on rate of heating.	07
Q.4	(b)	Enlist various types of battery charging methods. Explain any one of them in detail.	07
Q.5	(a)	(1) high frequency fluorescent lighting	08
	(b)	(2) Induction Cooking. With block diagram, explain working of speed control DC Motor  OR	06
Q.5	(a)	State motor drive applications. Discuss any two of them.	08
٠.٠	(b)	Explain utility of Simulation for Power Electronics systems.	06

1