

GUJARAT TECHNOLOGICAL UNIVERSITY**BE - SEMESTER-VI • EXAMINATION – SUMMER 2013****Subject Code: 162404****Date: 03-06-2013****Subject Name: Industrial Drives and Control-I****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Notations used have usual meaning.

- Q.1** (a) What is drive? Explain basic block diagram of DC drive system. **07**
(b) Discuss the speed/torque and torque/current characteristics of DC series motor. **07**

- Q.2** (a) Discuss types of motor duty. And write brief note on selection of DC motor. **07**
(b) A half wave controlled rectifier connected to a 150 V, 50 Hz source is supplying a resistive load of 10 ohm. If the delay angle is 30°, find (i) the maximum load current (ii) average load voltage (iii) RMS load current. **07**

OR

- (b) A step down chopper operates at a fixed frequency of 100 Hz from a 220 Vdc source supplying a load with 1 ohm and 10 mH inductance. If the output voltage is 60 V, find (i) t_{on} (ii) the average output current (iii) Draw the waveforms for output current and diode current. **07**

- Q.3** (a) Explain speed control of separately excited DC motor through full controlled converter. **07**
(b) Explain three phase controlled converter with neat diagram. Also draw appropriate waveforms. **07**

OR

- Q.3** (a) Discuss PLL based control of DC motor with block diagram. **07**
(b) Write brief note on permanent magnet motor drive. **07**

- Q.4** (a) Discuss modeling of DC motor controlled through armature voltage control. **07**
(b) Explain the need of PI control for DC drive system. **07**

OR

- Q.4** (a) Draw and Explain class A chopper circuit for DC motor. **07**
(b) Derive an expression for average output voltage of boost chopper circuit. **07**

- Q.5** (a) Discuss closed loop speed control of DC motor. Why current loop is to be introduced as an inner loop in closed loop operation. **07**
(b) Explain multi-phase chopper circuit. Discuss its merits and demerit. **07**

OR

- Q.5** (a) Explain two quadrant chopper circuit with neat diagram. **07**
(b) Explain dual converter circuit for DC motor. Also draw the relevant waveforms. **07**
