

Seat No.: _____

Enrolment No. _____

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-III • EXAMINATION – SUMMER • 2014

Subject Code: 130902

Date: 26-05-2014

Subject Name: Analog and Digital Electronics

Time: 02.30 pm - 05.00 pm

Total Marks: 70

Instructions:

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q-1** (a) What do you understand by the equivalent circuit of an Op-amp and also explain ideal voltage transfer curve with neat sketch. (07)
- (b) Explain the use of op-amp as a zero crossing detector with neat sketch. (07)
- Q-2** (a) Explain DeMorgan's Theorem with necessary truth table (07)
- (b) Write short note on R-S flip flop. (07)
- OR
- (b) Write short note on J-K flip flop. (07)
- Q-3** (a) With suitable example explain binary addition, subtraction, division and multiplication. (07)
- (b) Explain astable mode of operation of 555 timer. (07)
- OR
- Q-3** (a) Convert the following decimal numbers to binary. (07)
- (i) 23 (ii) 13
- (b) Convert hexadecimal number 3C to its decimal equivalent. (07)
- Q-4** (a) Draw circuit diagram of the full adder, write equations and also draw truth table and Explain it. (07)
- (b) Since sign-magnitude numbers are fairly easy to understand, why has 2's complement System becomes so widespread? (07)
- OR
- Q-4** (a) Convert the following binary numbers to decimal numbers. (07)
- (i) 00111
- (ii) 11001
- (iii) 10110
- (iv) 11110
- (b) Explain Analog to Digital Converter. (07)
- Q-5** (a) Define encoders, decoders, multiplexer and de-multiplexer Give application of Each. (07)
- (b) Define Register. Give its classifications. Explain any one classification. (07)
- OR
- Q-5** (a) What is schmittz'trigger? Explain in detail. (07)
- (b) Write short note on D-flip-flop. (07)
