Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

BE - SEMESTER-V • EXAMINATION - SUMMER • 2014

Subje	ect (	Code: 150903 Date: 19-06-2014	
•	: 10	Name: Power Electronics-I  .30 am - 01.00 pm  Total Marks: 70	
Institut	1. 2.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a) (b)	phase half wave rectifier assuming purely resistive load. Draw necessary waveform.	
Q.2	(a) (b)	Explain steady state V-I characteristics of power BJT. Also discuss the second breakdown phenomenon in brief.  Draw & explain dynamic turn-on characteristics of SCR.  OR	07 07
	<b>(b)</b>	Discuss the operation of buck-boost converter.	07
Q.3	(a) (b)	Explain two transistor analogy of an SCR. What are the methods of DC motor speed control? Explain single phase semi-converter DC motor drive.	07 07
Q.3	(a) (b)	OR  Explain RC firing circuit for SCR. Draw output voltage waveform for firing angle equal to 90°.  What do you mean by commutation of SCR? Explain any one method in brief.	07 07
Q.4	(a) (b)	With neat diagram & waveform explain UJT oscillator triggering.  Write a short note on voltage rating of SCR.  OR	07 07
Q.4	(a) (b)	A relaxation oscillator using a UJT is to be designed for triggering an SCR. The UJT has the following data $I_p = 0.6 \text{mA}, \ V_p = 18 \text{V}, \ V_v = 1 \text{V}, \ R_{bb} = 5 \text{K}\Omega, \ \eta = 0.72, \ C = 0.04 \mu\text{F}, \ \text{firing frequency is 2KHz, normal leakage current with emitter open is 4.2mA.}$ Compute the values of R, R1 & R2. Write a short note on protection of SCR.	07
Q.5	(a) (b)	What are the control strategies for chopper? Explain in brief.  Explain the operation of dual converter circuit.  OR	07 07
Q.5	(a) (b)	Explain regenerative braking control in DC machines using chopper circuit.  Explain the working of MOSFET.  ***********************************	07 07