

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**BE - SEMESTER-V • EXAMINATION – SUMMER • 2014**

**Subject Code: 152402****Date: 13-06-2014****Subject Name: Electrical Measurement & Electronics Instrument****Time: 10.30 am - 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Explain principle and operation of PMMC instrument. Derive torque equation for it. **07**  
(b) Explain the classification of Electrical and Electronics Instruments. **07**

- Q.2** (a) Explain the construction and working of Electrodynamometer type instruments. **07**  
(b) Explain construction, principle and operation of D'Arsonval Galvanometer. Derive torque equation for it. **07**

OR

- (b) State various types of errors in potential transformer. Explain how they can be reduced. **07**

- Q.3** (a) With neat diagram explain construction and operation of single phase energy meter. **07**  
(b) A moving coil ammeter has a fixed shunt of 0.02 ohm. With a coil resistance of  $R=1000\text{ohm}$  and a potential difference of 500mV across it, full scale deflection is obtained (a) To what shunted current does this correspond?(b) Calculate the value of R to give full scale deflection when shunted current I is (i)10A(ii)75A and (c) With what value of R is 40% deflection obtained with  $I=100\text{A}$ ? **07**

OR

- Q.3** (a) Explain the construction and characteristics of CT with its equivalent circuit and necessary phasor diagram. **07**  
(b) Calculate the Q factor and effective resistance of a circuit tuned to a frequency of 1.5MHz and having an effective capacitance of 150pF. In this circuit the current falls to 70.7% of its resonant value when the frequency of an emf of constant magnitude injected in series with the circuit deviates from the resonant frequency by 5kHz. **07**

- Q.4** (a) Explain the classification of resistance. List the methods for measurement of low resistance. Explain Kelvin Double Bridge using circuit diagram and necessary equation. **07**  
(b) Explain De Sauty Bridge using necessary circuit diagram, phasor diagram and equation. **07**

OR

- Q.4** (a) Explain Op-Amp voltage follower voltmeter. **07**  
(b) Explain working principle of rectifier type ammeter in detail. **07**

- Q.5** (a) Give different accessories for measuring instruments. Explain 1) RF demodulator probes 2) current probes. **07**  
(b) Explain Maxwell's bridge with necessary diagrams. **07**

OR

- Q.5** (a) Draw basic block diagram of a digital frequency meter. Discuss each block in details. **07**  
(b) Define Q factor of Inductor. Explain the working of Digital LCR Meter with neat Block diagram. **07**

\*\*\*\*\*