Seat No.:	Enrolment No.
Seat No	Emoniem No

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VI • EXAMINATION - SUMMER • 2014** 

	U	Code: 162405 Date: 26-05-2014			
Sul	Subject Name: Power Processing circuit -I				
	Time: 10:30 am - 01:00 pm Total Marks: 70				
Inst	ruction				
	1. 2.	1 1			
		Make suitable assumptions wherever necessary. Figures to the right indicate full marks.			
	٥.	right to the right indicate run marins.			
Q.1	(a)	Discuss 3-phase controlled rectifier with resistive load with necessary waveforms. Assume $\alpha = 45^{\circ}$ .	08		
	<b>(b)</b>	Compare:	06		
	, ,	<ul><li>(i) 1-phase and 3-phase rectifier</li><li>(ii) ZVS and ZCS</li></ul>			
Q.2	(a)	Describe modeling of an uncontrolled rectifier.	07		
<b>~</b>	(b)	Discuss current mode control of power supply in detail.	07		
	(,-)	OR			
	<b>(b)</b>	Explain working of input and output filter for a linear regulated power supply.	07		
Q.3	(a)	Analyze the operation of Jone's Chopper with necessary wave forms.			
	(b)	Analyze the operation of Jone's Chopper with necessary wave forms.  Draw a type $-A$ chopper circuit. It is operating at $2kHz$ from a $100 \text{ V}$ dc source has a load time constant of $6ms$ and load resistance of $10\Omega$ . Assume mean load voltage is $50 \text{ V}$ . Determine (i) Chopping period (ii) duty cycle . <b>OR</b>			
Q.3	(a)	Describe various control strategies for chopper circuit.	07		
•	<b>(b)</b>	Derive an expression for (i) average load voltage and (ii) rms load voltage for a single-phase one-pulse diode rectifier feeding RL load.	07		
Q.4	(a)	Write short note on: Sepic converter.	07		
<b>Q</b> ··-	(b)	Discuss with the help of power circuit operation of a half bridge converter. What are its limitations?	07		
		OR			
<b>Q.4</b>	<b>(a)</b>	Write short note on: Forward converter.	07		
	<b>(b)</b>	Classify non-isolated DC-DC converter and explain any one.	07		
Q.5	(a)	Discuss output rectifier and filter circuits for an isolated converter.	07		
-	<b>(b)</b>	Write short note on: Load resonant converter	07		
		OR			
Q.5	<b>(a)</b>	Discuss any one FOUR terminal IC based voltage regulator.	07		
	<b>(b)</b>	Write short note on: ZVS clamped voltage DC-DC converter	07		

\*\*\*\*\*