Seat No.:	Enrolment No.

Subject Code:170801

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII • EXAMINATION - SUMMER • 2014

Date: 22-05-2014

Subject Name: Power Electronics and Industrial Drives Time: 02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. **Q.1** (a) Briefly state and discuss the various schematics of single phase ac to ac 7 voltage controller. (b) Explain full wave controller with R-L load. Draw the necessary 7 wave-form. **Q.2** (a) Draw the schematic arrangement of full wave rectifier with R-L load and 7 back emf E. Draw its waveform for load voltage V_L and Load Current I_L . Write down the formulae for rms diode current I_r , and average diode current I_{d.} for discontinuous load current. Briefly explain the voltage protection by selenium diode and metal oxide 7 varistors (b) Briefly explain the gate driver circuits for thyristors. (a) What is VSI? Describe the operation of single phase half bridge VSI. 0.3 7 Also state the switching state table for the same. Briefly discuss the operation of on off controller with neat sketch of its 7 waveform **Q.3** .Explain the operation of 4 switch Single Phase Inverter with usual 7 notations. What is cyclo converter? state the area of its application. Briefly discuss 7 the operation of single phase cyclo converter along with its voltage and current waveform for resistive load. (a) Explain the selective harmonic elimination technique for VSI. 7 **Q.4** (b) Briefly discuss the 120 degree operation of inverter circuit with 7 appropriate waveforms. OR (a) Discuss the class B operation of Chopper Circuit. 7 **Q.4** (b) Give comparison between current source inverter and voltage source (a) Explain slip-power recovery by Static Scherbius method for speed 7 **Q.5** control of induction motor. Explain V/f control of induction motor drives Give its merits and 7 demerits. OR (a) Discuss the rotor voltage control for slip ring induction motor 7 Q.5 Discuss about choice of AC and DC drive in detail 7
