C AT	T I AN
Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VII • EXAMINATION - SUMMER • 2014** 

Su	bject	Code: 170803 Date: 05-06-2016 Name: Electrical and Electronics Measuring Instruments	
	me: U tructio	02:30 pm - 05:00 pm Total Marks: 70	0
1115	1. 2.	Attempt all questions.	
Q.1	(a)	What is measurement standard? List out different types of standard. Explain voltage standard in brief.	07
	<b>(b)</b>	Define: (1) Accuracy (2) Precision (3) Resolution (4) Sensitivity (5) Threshold (6) Drift (7) Reproducibility.	07
Q.2	(a)	Describe the various operating torque needed for proper operation of an analog indicating instrument. Draw the neat sketch & explain in detail of eddy current damping torque in analog instrument.	07
(	<b>(b)</b>	Explain the construction and working of an electrodynamometer type of wattmeter.	07
	(b)	OR A resistance of approximate value of 80 ohm is to be measured by voltmeter-ammeter method using a 1 An ammeter having resistance of 2 ohm and 50 V voltmeter having a resistance of 5000 ohm. (a) Suggest which two method should be used? (b) Supposing in the suggested method I=0.42A and V=35.5v what is the resulting error if the accuracy of the instrument is 0.5% at full scale and the error are standard deviations.	07
Q.3	(a)	Describe the working of Hay's bridge for the measurement of inductance.  Derive the condition for balance and draw the phasor diagram.	07
	<b>(b)</b>	State different method for the measurement of unknown capacitance. <b>OR</b>	07
Q.3	(a) (b)	Explains the PMMC Type Ammeter With Torque Equation.  Explains the electrodynamometer type low power factor wattmeter.	07 07
Q.4	(a)	Draw the phasor diagram & derive the expression for deflecting torque & braking torque in single phase induction type energy meter.	07
	<b>(b)</b>	Explain Maxwell's bridge for measurement of unknown inductance. Also determine condition for balance with phasor diagram.	07
		OR	
Q.4	(a)	Derive expression for unknown resistance in case of Kelvin's double bridge.	07
	<b>(b)</b>	Describe the working of Hay's bridge for the measurement of inductance. Derive the condition for balance and draw the phasor diagram	07
Q.5	(a)	Describe with the help of neat diagram the loss of charge method to determine the insulation resistance of a short length of cable and derive an expression for determination of insulation resistance.	07
	<b>(b)</b>	Explain construction and working of potential transformer. Also explain ratio and phase angle error.	07

- Q.5 (a) Explain with the help of neat diagram the working of a digital voltmeter.
  - (b) Explain with the help of a block diagram the working of a spectrum analyzer? 07 Where is spectrum analyzers commonly used?

\*\*\*\*\*

**07**