Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII • EXAMINATION - SUMMER • 2014

Subject Code: 171002		Code: 171002 Date: 03-06-201	Date: 03-06-2014	
Tir	•	Name: Power Electronics 2:30 pm - 05:00 pm Total Marks: 7	0	
		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a)	List the different members of the thyristor family and draw their characteristics and explain in brief.	07	
	(b)	Explain single phase half wave rectifier with suitable circuit and waveform.	07	
Q.2	(a) (b)	Discuss briefly the parallel operation of MOSFETs Explain the safe operating areas of an IGBT. OR	07 07	
	(b)	A three –phase fully- controlled bridge converter is connected to three-phase a.c. supply of 400 V, 50Hz and operates with a firing angle $\alpha = \pi/4$. The load current is maintained at 10A and the load voltage is 360 V. Compute: (i) Source inductance, L_s (ii) Load resistance, R (iii) Overlap angle, μ .	07	
Q.3	(a)	Explain the various techniques of improving power factor in three phase controlled converters.	07	
	(b)	Explain the DC Chopper's principal of operation . OR	07	
Q.3	(a)	A DC Chopper operates on 230 V dc and frequency of 400Hz; feed an R-L load. Determine the ON time of the chopper for output of 150 V.	07	
	(b)	Briefly discuss the switching behavior of a GTO.	07	
Q.4	(a) (b)	Explain single phase full bridge inverter. A single-phase half bridge inverter has a resistive load of $R=3\Omega$ and the dc input voltage E_{dc} =24 Volts. Determine: (i) IGBT ratings (ii) Total Harmonics distortion THD (iii) The distortion factor DF (iv) The Harmonics factor and DF of the lowest order harmonic.	07 07	
Q.4	(a)	OR Discuss the pulse width modulated inverter.	07	
Ų. 4	(a) (b)	Explain three phase bridge inverter.	07	
Q.5	(a) (b)	Explain the operation of UPS system Explain switched mode power supplies. OR	07 07	
Q.5	(a) (b)	Compare dielectric heating with induction heating Draw and explain the operation of automatic battery charger with trickle charging arrangement.	07 07	
