0.2

0.3

Q.3

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VII • EXAMINATION - SUMMER • 2014 Subject Code: 172401 Date: 22-05-2014 Subject Name: Power Electronics Systems Modeling Time: 02:30 pm - 05:00 pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Draw and Explain the block diagram of Power Electronics System with 0.1 (a) 07 reference to modeling. (b) State inductor volt-second balance principle and explain its use in buck 07 converter. Explain DC transformer model with necessary equations and figures. 06 (a) Find out the steady state output voltage for a buck chopper using small-ripple (b) 08 approximation. Draw necessary diagrams & waveforms. Also derive the equation for voltage conversion ratio M(D) and draw it's graph. OR For a given buck converter, if the input voltage is 50 V, Mark Space Ratio is 08 (b) 0.25. Switching frequency is 100 kHz and load resistance is 10 Ω , calculate the value of V_0 and I. Also find out the value of C such that the peak output voltage ripple ΔV is 5% of V₀. 07 (a) Discuss different types of modeling methods with their merit and demerits. List the major steps of engineering design process. Explain each in brief. 07 (b) OR What do you mean by small signal approximation? Explain with appropriate (a) 06 example. Why is AC modeling required? Discuss non-linearity in electrical system. (b) **08** Explain perturbation and linearization w.r.t. power electronics. Develop the state space model of a buck converter. Draw necessary figures. 08

Q.4 (a) Define the following: Modeling, Controllability, SISO, Normalization, Impulse 06 (b) Response, Linerization

OR

- Explain the difference between ideal and physical models of AC transformer. **O.** 4 (a) 06 Draw neat diagrams.
 - (b) Develop the state space model of a boost converter along with necessary figures. **08**
- What is Canonical Circuit Model? Explain the manipulation of buck-boost 07 **Q.5** (a) converter model into canonical form.
 - Explain the graphical construction of series impedances using a series R-C (b) 07 network.

OR

- Explain the close loop speed control of DC motor using power electronics 07 Q.5 (a) converter.
 - Explain the state space model of a full bridge inverter. 07 (b) *********