Seat No.: _

Enrolment No.__

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-VIII • EXAMINATION – SUMMER 2014

Subject Code: 180907 Date: 27-05-2014 Subject Name: Advanced Power Electronics-II Time: 10:30 am TO 01:00 pm **Total Marks: 70** Instructions: 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. Q.1 State types of HVDC systems and explain each in brief. 07 **(a)** Define FACTs systems and state its possible benefits in Emerging Transmission 07 **(b)** Network. Showing well labeled figure, explain the combined converter characteristics of 07 Q.2 **(a)** the HVDC system. Explain each part of Characteristics. Explain basic principle of shunt compensation used for transmission line. How **(b)** 07 it is useful to improve performance of system. OR Explain basic principle of series compensation used for transmission line. How 07 **(b)** it is useful to improve performance of system. Explain working of Synchronous Condensor. How same type of compensation **Q.3** 07 (a) can be achieved by using STATCOM. Explain working of STATCOM. Giving circuit diagram, explain the working of combined TSC-TCR 07 **(b)** compensator circuit. Draw its steady state voltage - reactive power characteristics. OR Draw the circuit diagram and explain the working of Static Synchronous Series Q.3 07 **(a)** Compensator (SSSC). Draw the circuit diagram and explain the working of Thyristorised Controlled **(b)** 07 Reactor (TCR). Explain effect of overlap angle on the performance line commutated converter. **Q.4** 07 **(a)** Also discuss the parameters, on which overlap angle depends. Stating basic assumptions, derive the output DC voltage equation for 6-pulse **(b)** 07 line commutated converter. Also prove that power factor of converter is proportional to cosine of firing angle. OR **Q.4** Explain basic requirements of firing circuits used in HVDC system. Also 07 **(a)** explain types of firing schemes used in HVDC system. Giving block diagram, explain working of Power Controller. 07 **(b)** Q.5 Explain the working of Voltage Source Converter operation and its principle. 07 **(a)** Showing circuit diagram, explain working of Unified Power Flow Controller **(b)** 07 (UPFC). OR Showing block diagram, explain working of Constant Extinction Angel Q.5 07 **(a)** Controller used in Converter Control of HVDC system. Compare the performance of static compensators TCR and TSC. 07 **(b)**
