

GUJARAT TECHNOLOGICAL UNIVERSITY
BE SEMESTER– 1st/2nd (OLD SYLLABUS) EXAMINATION – SUMMER 2015

Subject Code:110005**Date:16/06/2015****Subject Name: Elements of Electrical Engineering****Time: 10:30 am - 01:00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Derive equivalent resistances for delta to star transformation. **05**
 (b) Derive an expression for temperature coefficient at temperature t , $\alpha_t = \alpha_0 / (1 + \alpha_0 t)$. Where notations have usual meanings. **05**
 (c) A 100 A current is shared by three resistances connected in parallel. The resistor wires are of the same material and have their length in the ratio 2:3:4 and their cross sectional area in the ratio 1:2:3. Determine the current in each resistor. **04**
- Q.2** (a) Define & explain following terms:
 (1) Magneto Motive Force (M.M.F.) (2) Reluctance (3) Magnetic Field Intensity. **03**
 (b) Derive equation for energy stored in a capacitor **05**
 (c) A 8 μF capacitor is connected with 0.5 $\text{M}\Omega$ resistor across a 200 V d.c supply. Calculate:(i)the time constant,(ii)the initial charging current,(iii)time taken for the p.d across the capacitor to grow to 160 V and(iv)the current and voltage across the capacitor in 4 second after it is connected to the supply. **06**
- Q.3** (a) Obtain the relation $L = (L_1 L_2 - M^2) / (L_1 + L_2 + 2M)$ for equivalent inductance when two inductors are connected in parallel such that the mutually induced emf opposes the self induced emf. **07**
 (b) Compare similarities and dissimilarities between electrical and magnetic circuits. **07**
- Q.4** (a) Prove that current in pure inductive circuit lags its voltage by 90° . **07**
 (b) Define the following terms with respect to AC waveforms (1) phase (2) Time period **04**
 (c) A certain waveform has a form factor of 1.2 and a peak factor of 1.5.If the maximum value is 100,find the r.m.s value and average value. **03**
- Q.5** (a) Explain series resonance circuit. Draw resonance curve. **07**
 (b) Established relationship between line and phase voltages and currents in balanced delta connection. Draw complete phasor diagram of voltages and currents. **07**
- Q.6** (a) Explain two wattmeter method for 3-phase power measurement. **07**
 (b) What is Battery? Explain the construction and working of any battery. **03**
 (c) Draw & explain staircase wiring with necessary sketch. **04**
- Q.7** (a) Explain construction of cable. **05**
 (b) What is an electric shock? Why grounding is required? **05**
 (c) State types of fuse and explain any one. **04**
