GUJARAT TECHNOLOGICAL UNIVERSITY BE- SEMESTER- IV EXAMINATION-SUMMER 2015

Subject Code:142402 Date: 08/				
Subject Name: Fundamentals of Power Electronics Time: 10.30am-01.00pm Total Mar Instructions:				
1115		Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks.		
Q.1	(a) (b)	Discuss utility of latching current and holding current in Power Electronics. Describe construction & working of SCR. Analyze it's performance using two transistor Analogy.	02 05	
	(c)	Draw symbols and V-I characteristics of (a) Diode (b) DIAC (c) Power BJT (d) UJT (e) TRIAC (f) Power MOSFET (g) IGBT	07	
Q.2	(a)	What do you mean by "Power Electronic System"? Draw & explain the block diagram of Power Electronic System. Also, enumerate the advantages of Power Electronic System.	07	
	(b)	Write a detailed note on TURN ON Methods of SCR. OR	07	
	(b)	Draw the Power circuit, Symbol & V-I characteristic of UJT. Derive the expression for periodic time T of UJT relaxation oscillator.	07	
Q.3	(a)	Draw and explain equivalent circuit and transient response of Fast Recovery diode.	07	
	(b)	Define TRIAC. Enlist all triggering modes of TRIAC and explain the most Sensitive mode.	07	
		OR	~-	
Q.3	(a)	What are the benefits of IGBT over SCR. Draw the structure, symbol & output characteristics of IGBT?	07	
	(b)	Draw and explain schematic construction, symbol and V-I characteristic of LASCR.	07	
Q.4	(a) (b)	Explain dv/dt and di/dt protection of SCR. Define Chopper. Explain Principles of operation of STEP-UP/DOWN Chopper and Derive equation for Output Voltage. OR	07 07	
Q.4	(a)	Explain with the help of neat power diagram and associated waveforms, the operation of 1-phase half-wave controlled converter with Resistive and Inductive load.	07	
	(b)	Discuss principle and working of SMPS with the help of block diagram.	07	
Q.5	(a)	Define and classify Inverters. Draw and explain single phase MC-MURRAY Inverter circuit with voltage and current waveforms.	07	
	(b)	What is Cycloconverter? Explain working and application of it. OR	07	
Q.5	(a)	Explain the basic principle and working of single-phase step down cycloconverter.	07	
	(b)	Write the principle of inverter. Enlist the various types of inverter circuits. Explain the operation of $1-\emptyset$ bridge inverter.	07	
