Seat No.:	Enrolment No.
-----------	---------------

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-V • EXAMINATION - SUMMER • 2015

	-	ct Code: 152402 Date: 05-05-201 ct Name: Electrical Measurement & Electronics Instrument	.5
T	•	02.30 pm - 05.00 pm Total Marks: 7	0
		 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 	
Q.1	(a) (b)	Explain the calibration of voltmeter and ammeter using potentiometer. Define following. 1. Drift 2. Reproducibility 3. Accuracy 4. Fidelity 5. Resolution 6. Backlash	08 06
Q.2	(a) (b)	Draw the equivalent circuit and the phasor diagram of Current Transformer. Derive the equation for actual transformation ratio K_{act} . Explain in brief the low capacitance, high voltage and RF demodulator Probes.	07 07
	(b)	OR Define measurement. Draw the diagram of generalized measurement system. Explain the standards of measurement in detail.	07
Q.3	(a) (b)	Explain the construction and working of D'Aasonval Galvanometer. Explain the shunt type ohmmeter and its design.	07 07
Q.3	(a) (b)	OR Explain the construction and working of Dynamometer type instruments. Explain the op-amp voltage follower and op-amp amplifier type voltmeters.	07 07
Q.4	(a) (b)	Write a technical short note on : Dual-slope Integrator type DVM. Explain the construction and working of poly phase energy meter. OR	07 07
Q. 4	(a) (b)	Explain the Digital frequency meter with block diagram. Explain how the power loss in pressure coil is compensated in electrodynamic wattmeter. Explain the low power factor meter.	07 07
Q.5	(a)	Explain the Kelvin double bridge method of measurement of low resistance in detail.	07
	(b)	Explain the Hay's bridge for measurement of inductance. OR	07
Q.5	(a) (b)	Explain the loss of charge method of measurement of high resistance in detail. Explain the Schering's bridge for measurement of capacitance.	07 07
	(0)	Explain the sellering 5 ortuge for measurement of capacitance.	U/
