GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER-V • EXAMINATION – SUMMER • 2015

Subject Code: 152405 Date: 15/0 Subject Name: Power Electronics Applications			5/2015	
Tir	Time: 02.30pm-05.00pm Total Mark		ks: 70	
Insi	1. 2. 3.	Attempt all questions. Make suitable assumptions wherever necessary.		
Q.1	(a) (b)	Write a detailed note on Ideal switch characteristics. Fill in blanks. 1 works as a relaxation oscillator.	07 02	
	(c)	2 Triggering is the most commonly used method for triggering SCRs. Write a note on TURN ON methods of SCR.	05	
Q.2	(a) (b)	Draw & explain block diagram of Power Electronics System. Explain two transistor Analogy of SCR.	07 07	
	(b)	OR Draw & explain construction, symbol & V-I characteristics of a DIAC. Also list out application of DIAC.	07	
Q.3	(a)	A three-phase half wave controlled rectifier has a supply voltage of 200V/phase. Determine the average load voltage for firing angle of 0°, 30°, 60°, assuming a thyristor volt drop of 1.5V and continuous load current.	07	
	(b)	Write a short note on Buck Regulator. OR	07	
Q.3	(a) (b)	What is basic requirement of UPS? Classify & explain types of UPS. With necessary waveforms discuss cycloconverter.	07 07	
Q.4	(a) (b)	Write a detailed note on battery operated vehicle. Explain Induction Cooking, space heating & Air conditioning applications of Power electronics with suitable diagrams OR	07 07	
Q.4	(a)	Draw & explain block diagram of motor drive. Enlist & explain advantages & disadvantages of variable speed drives.	07	
	(b)	Explain working & principle of High frequency fluorescent lighting. Also explain V^2 -I characteristics.	07	
Q.5	(a) (b)	Differentiate: Static circuit breaker – Mechanical circuit breaker. Draw & explain circuit configurations of electric arc welding. OR	07 07	
Q.5	(a) (b)	What is HVDC? Explain with suitable block diagram. Write a detailed note on Electronics timer.	07 07	
