

GUJARAT TECHNOLOGICAL UNIVERSITY
BE - SEMESTER-VI • EXAMINATION – SUMMER 2015

Subject Code: 160801**Date:01/05/2015****Subject Name: Integrated Circuits & Application****Time:10.30AM-01.00PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Draw and explain the functional block diagram of IC 555. **07**
 (b) Explain the following parameters of OPAMP (i)Input offset voltage **07**
 (ii)Input bias current (iii)CMRR (iv)Slew rate (v)PSRR
- Q.2** (a) List the advantages of negative feedback, explain any one application of **07**
 OPAMP in open loop configuration with output waveforms.
 (b) Define Error voltage and Derive its equation for Op-Amp. **07**
OR
 (b) Derive the expression for Voltage gain (A_V) and input resistance with **07**
 feedback (R_{IF}) for voltage shunt feedback amplifier.
- Q.3** (a) Explain Schmitt trigger circuit using OPAMP. **07**
 (b) What is V to I converter? Explain the circuit of low voltage DC voltmeter. **07**
OR
- Q.3** (a) Explain the practical integrator circuit. Also draw its frequency response **07**
 (b) Explain Instrumentation Amplifier using transducer bridge with its **07**
 application.
- Q.4** (a) Describe a sample and hold circuit and give its applications. **07**
 (b) Explain a circuit using OPAMP which can produce triangular waveform at **07**
 its output.
OR
- Q.4** (a) Explain the application of PLL in FSK demodulation. **07**
 (b) Explain IC 555 as a Monostable multivibrator .Give the expression for the **07**
 time delay.
- Q.5** (a) Explain Astable multivibrator using Op-Amp. **07**
 (b) Draw the block diagram of PLL and explain each block. **07**
OR
- Q.5** (a) Draw and Explain the block diagram representation of a typical Op-Amp. **07**
 (b) Draw and explain a 3 input summing, scaling and averaging circuit using **07**
 OPAMP.
