Seat No.:	Enrolment No.

Subject Code:160905

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VI • EXAMINATION - SUMMER • 2015

Date:12/05/2015

\mathbf{T}	•	t Name:Electrical and Electronic Measurement 10.30am-01.00pm Total Marks: 7 ions:	' 0
	2	 Attempt all questions. Make suitable assumptions wherever necessary. Figures to the right indicate full marks. 	
Q.1	(a)	State the methods for measurement of high resistance and explain any one in detail.	07
	(b)	Explain the following terms, 1. Sensitivity 2. Accuracy 3. Drift 4. Precision 5. Linearity 6. Resolution 7. Stability.	07
Q.2	(a)	Explain Maxwell's inductance-capacitance bridge with circuit diagram and phasor diagram. Derive the condition for balance.	07
	(b)	Describe sources and null detector used in A.C. bridge	07
		OR	
	(b)	Derive equation for De sauty's bridge for capacitor measurement with diagram.	07
Q.3	(a)	Draw the circuit of Kelvin's double bridge used for measurement of low resistance. Derive the condition for balance.	07
	(b)	Explain Murray loop test for localization of ground and short circuit fault in cables.	07
		OR	
Q.3	(a)	Describe the varley loop test for localization of ground and short circuit fault in cables.	07
	(b)	Explain fall of potential method for measurement of earth resistance.	07
Q.4	(a)	Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expression for ratio and phase angle errors.	07
	(b)	Discuss principle and working of digital LCR meter.	07
		OR	
Q.4	(a) (b)	Describe the method for determination of B-H curve of magnetic material. Explain comparision method of testing of potential transformer.	07 07
Q.5	(a)	Explain Harmonic distortion analyser.	07
	(b)	Explain constructional features and working of flux meter.	07
		OR	
Q.5	(a) (b)	Discuss applications of spectrum analyser. State the requirements of a good instrumentation amplifier.	07 07
