Seat No.:	Enrolment No.

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

**BE - SEMESTER-VI • EXAMINATION - SUMMER • 2015** 

•		Code: 162404 Date:14/05/2015  James Industrial Drives & Control 1	
•	e:10.	Name: Industrial Drives & Control-1 30am-01.00pm Total Marks: 70	
THS CT C	1. 2.	Attempt all questions.  Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.	
Q.1	(a) (b)	Draw & Explain Basic Block Diagram of DC drive. List Advantages & Disadvantages of DC Drive.	07 07
Q.2	(a) (b)	Write a short note on Ward Leonard System.  Derive Torque equation of DC motor indicating Dynamics of Electrical Drive.	07 07
		OR	
	<b>(b)</b>	List various methods of speed control of dc shunt motor. Explain any two in detail	07
Q.3	(a)	Explain braking of separately excited dc Motor using chopper circuit with waveforms.	07
	<b>(b)</b>	Draw & Explain waveforms of 1- $\Phi$ fully controlled converter with freewheeling diode for Separately Excited DC Motor.  OR	07
Q.3	(a) (b)	Explain Motoring operation of chopper controlled separately excited dc Motor. Draw circuit diagram & waveforms for 3- $\Phi$ fully controlled converter with $\alpha = 30^{\circ}$ for Separately Excited DC Motor. Derive the equation for output voltage.	07 07
Q.4	(a) (b)	Discuss circulating type dual converter with necessary diagram. Explain four quadrant operation of chopper for RLE load.	07 07
		OR	
Q.4	(a) (b)	With the help of Block diagram explain Closed loop control for DC drive.  Differentiate Permanent Magnet Drive & Servo Motor Drive.	07 07
Q.5	(a)	A 80KW, 440V, 800 rpm D.C. motor is operating at 600 rpm & developing 75% of rated torque is controlled by 3-Φ, six pulse thyristor converter. If the back emf at rated speed is 410 V, determine the triggering angle of the converter. The input to the converter is 3-Φ, 415V, 50Hz supply.	07
	<b>(b)</b>	Explain Micro computer control of DC Drives using block Diagram.	07
		OR	
Q.5	(a)	An RLE type load is operating in a chopper circuit from a 400V D.C. supply. For the load $L = 0.05H \& R=0 \&$ for a duty cycle of 0.3, find the chopping frequency to limit the amplitude of the load current excursion to 8A.	07
	<b>(b)</b>	Short Note on PLL based DC drive.	07

\*\*\*\*\*