1

GUJARAT TECHNOLOGICAL UNIVERSITY

BE - SEMESTER-VII • EXAMINATION - SUMMER • 2015 Date: 08/05/2015

Subject code: 172402 Subject Name: IDC-II

Time: 02.30pm-05.00pm

Instructions:

- 1. Attempt all questions.
- 2. Make suitable assumptions wherever necessary.
- 3. Figures to the right indicate full marks.
- (a) Describe the analysis of Induction Motor with 1) Unbalanced rotor impedances 0.1 07 2) Non-sinusoidal voltage supply.
 - (b) Explain CSI control for IM and compare CSI with VSI giving three points.
- Q.2 (a) Explain stator voltage control of IM along with the torque speed characteristics. Also 07 draw the block diagram indicating the closed loop control of stator voltage using a proper power electronics modulator.
 - (b) Explain the concept of variable frequency control of IM drive. Why is V/F control 07 preferred over variable frequency control? Give proper reasons.

OR

- **(b)** Explain Static Scherbius Drive with a neat diagram and derive the speed-torque relation 07 for the same.
- 0.3 Draw and explain the block diagram of Open loop Volts/Hertz control of Synchronous 07 (a) Machine drives.
 - **(b)** A 400 V, 50 Hz, 6 pole, Y-connected IM has the following parameters per phase 07 referred to the stator: $R_s = 0.4 \Omega$, $R'_r = 0.2 \Omega$, $X_s = X'_r = 1.5 \Omega$, $Xm = 30\Omega$. If the motor running at 960 rpm is controlled by variable frequency control at a constant flux of rated value, calculate 1) The rated torque.

2) Motor speed at half the rated torque and 25 Hz.

OR

- Explain Self-controlled synchronous motor drive using load commutated thyristor 0.3 07 (a) inverter.
 - Derive the expression for flux vector estimation by Current Model. 07 **(b)**

| Q.4 | (a) | Describe the Bridge Converter and Split Rail Converter for SRM. | 07 |
|-----|-------------|---|----|
| - | (b) | Explain the basic principle of sensor less control of Induction Motor Drives. | 07 |
| | | OR | |
| Q.4 | (a) | Write a short note on: 1) Sinusoidal PMAC motor drives 2) Trapezoidal PMAC motor drives | 07 |
| Q.4 | (b) | Explain the basic principle of DTFC for Voltage fed PWM inverter drives. | 07 |
| Q.5 | (a) | Derive the stator reference model of Induction Motor in Arbitrary Reference Frames. | 07 |
| | (b) | Explain block diagram of feed-forward vector control for IM. | 07 |
| | | OR | |

- (a) Explain the need of dynamic modeling of Induction Machines giving necessary equations **Q.5** 07 and figures. Also state the assumptions made to derive the dynamic model. 07
 - Explain block diagram of feedback vector control for IM. **(b)**

Total Marks: 70

07

Enrolment No.