| Seat No.: | Enrolment No. |
|-----------|---------------|
|           |               |

## **GUJARAT TECHNOLOGICAL UNIVERSITY**

|            |            | BE - SEMESTER-VIII • EXAMINATION – SUMMER • 2015   |           |
|------------|------------|--|-----------|
| Su         | bject      | Code: 182405 Date:05/05/201:   | 5         |
| Su         | bject      | Name: Digital Control of Power Processing Circuits   |           |
| Ti         | me:10      | 0.30AM-01.00PM Total Marks: 7  | <b>70</b> |
| Ins        | tructio    |  |           |
|            |            | Attempt all questions.   |           |
|            | 2.<br>3.   | Make suitable assumptions wherever necessary.  Figures to the right indicate full marks.   |           |
|            | ٥.         | rightes to the right material marks.   |           |
| Q.1        | (a)        | Draw and explain in brief, the principle of operation of full bridge VSI along with the required basic components.                                 | 07        |
|            | <b>(b)</b> | Discuss about the digital PWM technique and compare it with analog PWM technique.  | 07        |
| Q.2        | (a)        | Compare analog and digital control. Explain the importance of digital control in modern power electronics.   | 07        |
|            | <b>(b)</b> | Explain low level control technique of VSI using naturally sampled PWM.  OR  | 07        |
|            | <b>(b)</b> | Explain low level control technique of VSI using uniformly sampled PWM.  | 07        |
| Q.3        | (a)        | Explain the simplified dynamic model of delays.  | 07        |
|            | <b>(b)</b> | Draw and explain dead beat current control loop with necessary equations.  OR  | 07        |
| Q.3        | (a)<br>(b) | Explain the discretization strategies of proportional integral controller.  Draw and explain the hysteresis current control hardware organization. | 07<br>07  |
| Q.4        | (a)        | Compare linear current control by PI controller with digital current control by PI controller.   | 07        |
|            | <b>(b)</b> | Discuss the effects of the computation delay. How it can be minimized?  OR   | 07        |
| <b>Q.4</b> | (a)<br>(b) | Discuss aliasing and its effects on signals.  Draw and explain the typical organization of 3-Φ VSI SVM based controller.                           | 07<br>07  |
| 0.5        |            |  |           |
| Q.5        | (a)<br>(b) | Explain the large and narrow bandwidth controllers.  Draw and explain the typical organization of Active Power Filter.                             | 07<br>07  |
|            | (D)        | OR   | U/        |
| Q.5        | (a)        | Explain DFT based voltage controller.  | 07        |
|            | <b>(b)</b> | Explain Quantization and Arithmetic noise.   | 07        |

\*\*\*\*\*