Seat No.:		No.: Enrolm	ent No		
	BE	GUJARAT TECHNOLOGICAL UNI SEMESTER- 1 st /2 nd (NEW SYLLABUS) EXAMINAT		R 2015	
_		Code: 2110005 Name: Elements of Electrical Engineering	Date:16/06/2015		
Time: 10.30am-01.00pm		.30am-01.00pm	Total Marks: 70		
Instruc	1. 2.	s: Question No. 1 is compulsory. Attempt any four out of rema Make suitable assumptions wherever necessary. Figures to the right indicate full marks.	ining Six question	5.	
Q.1				MARKS	
Ų.1	(a)	Objective Question – select only one option out of four	r (MCQ)	07	
	1.	The material used for fuse should have [a] low melting point & high conductivity [b] low melting point & low conductivity [c] high melting point & high conductivity [d] high melting point & low conductivity			
	2.	Earthing is necessary to [a] avoid risk of fire due to earth leakage [b] avoid electric shock to human body [c] both [a] & [b]			
	3.	[d] either [a] or [b]MCB provides protection against[a] short ckt.[b] overload[c] earth fault			
	4.	[d] all of the above The choke in tube light wiring provides [a] high current [b] high resistance [c] high impulse voltage			
	5.	[d] low reactanceWhich type of capacitor is used generally in fan?[a] ceramic[b] Electrolytic[c] mica			
	6.	[d] none of above The meter used at our premises measure [a] voltage [b] current [c] power			
	7.	[d] energy The frequency of DC supply is [a] 50 Hz [b] 1 Hz			

[c] 0 Hz

[d] none of above

	(1) Measuring range of ammeter can be extended by using		
	(a) high value of series resistance (b) low value of shunt resistance		
	(c) low value of series resistance (d) high value of shunt resistance		
	(2) Full name of MCB is		
	(a) Miniature circuit breaker (b) Minimum circuit breaker		
	(c) Maximum circuit breaker (d) None of the above		
	(3) Voltmeter always connected is in a circuit.		
	(a) Parallel (b) series (c) Both (a) & (b) (d) None of the above		
	(4) Unit of magneto motive force (mmf) is		
	(a) Weber (b) AT (c) Voltage (d) Tesla		
	(5) Average value of a.c. voltage =× Vm		
	(a) 1.414 (b) 0.707 (c) 0.637 (d) 1.5		
	(6) Unit of potential difference is		
	(a) voltamp (b) watt (c) ampere (d) voltage		
	(7) Value of form factor(Kf) is		
	(a) 0.707 (b) 1.414 (c) 0.637 (d) 1.11		
	(a) 0.707 (b) 1.111 (c) 0.037 (d) 1.11		
(b) 1.	Objective Question – select only one option out of four (MCQ) The unit of conductivity is [a] Siemens / m [b] Siemens-m [c] mho [d] mho-m	07	
2.	If relative permittivity is 5, then it's absolute permittivity is [a] $5 / \triangleleft \bigcirc$ [b] $5 \triangleleft \bigcirc$ [c] $\triangleleft \bigcirc / 5$ [d] 8.854×10^{-12}		
3.	The unit of permeance is [a] AT / Wb [b] Wb / AT [c] Henry [d] either [b] or [c]		
4.	[d] either [b] or [c] Q-factor of a coil means [a] Higher voltage magnification [b] Higher selectivity of the tuning coil [c] either [a] or [b] [d] both [a] and [b]		
5.	For a series resonance condition of a AC circuit current is [a] minimum [b] maximum [c] zero [d] infinity		
6.	For zero power factor load of 3-phase ckt.,if we measure the power by 2-wattmeter method then readings of wattmeters are		

[a] one wattmeter shows zero reading

	7.	 [b] equal & +ve sign [c] equal & opposite sign [d] both shows zero reading The gas used in sodium vapour lamp is [a] argon [b] nitrogen [c] neon [d] methane 	
Q.2	(a) (b)	State and explain kirchoff's voltage and current laws. Analyze Series and parallel circuit having resistors only as elements and state the results	03 04
	(c)	Derive the equations to translate a passive electric circuits from star network to delta network configuration with diagram.	07
Q.3	(a) (b)	State and explain coulomb's law of Electrostatics. A capacitor of 0.1 μF is charged from a 100 V battery through a series resistance of 1000 Ω. Find [1] Time constant [2] Charge received during this time [3] Initial rate of charging	03 04
	(c)	[4] the rate of charging when the charge is 63.2 % of final charge. Analyze the series and parallel connection of capacitor and prove the equations. Also find out the equation for energy stored in capacitor.	07
Q.4	(a) (b)	State and explain faraday's laws of electromagnetic Induction. If a coil of 150 turns is linked with a flux of 0.01 Wb, when carrying a current of 10 A. Calculate [1] the inductance of the coil [2] the induced e.m.f, if this current is uniformly reversed in 0.01 second.	03 04
	(c)	Analyze magnetic and electric circuits by similarities and differences	07
Q.5	(a)	Define the following for AC circuits: [1] R.M.S. value [2] Average value	03
	(b)	 [3] Power factor A resistance of 20 Ω, an inductance of 0.2 H and a capacitance of 100 μF are connected in series across 220 V,50 Hz supply. Find [1] Impedance [2] Voltage across R,L & C [3] Power factor & angle of lag [4] Active & apparent power 	04
	(c)	Prove the condition of resonance for R-L-C series AC circuit. Also analyze the phenomena with the help of graph.	07
Q.6	(a)	Explain in brief the following for 3-phase AC circuit: [1] Phase sequence [2] Line voltage [3] Phase voltage	03
	(b)	A Δ-connected balanced 3-phase load is supplied from 400 V , 3-phase mains. The line current is 20 A & the power taken by load is 10 MW. Find [1] Impedance in each branch	04

		[2] Power factor of the load[3] Line current & power consumed, if same load is connected in star.	
	(c)	Prove the equation for measurement of Electrical power in 3-phase circuit by two wattmeter method. Also draw phasor diagram.	07
Q.7	(a)	Explain in brief the following. [1] A-h & W-h capacity of a battery [2] Rating of MCB [3] Lumens	03
	(b)	Discuss the types of cables used for residential and commercial wiring.	04
	(c)	What do you mean by earthing? Analyze earthing concept with the help of a device-ELCB (Earth leakage circuit breaker) used at our residence	07
