Seat No.:	Enrolment No.

GUJARAT TECHNOLOGICAL UNIVERSITY BE - SEMESTER- III (NEW) EXAMINATION - SUMMER 2015

Subject Code: 2130902 Date:29/05/2015 **Subject Name: Analog Electronics** Time: 02.30pm-05.00pm **Total Marks: 70 Instructions:** 1. Attempt all questions. 2. Make suitable assumptions wherever necessary. 3. Figures to the right indicate full marks. **4.** Parameters of 741 IC are: A (open loop gain) = 2×10^5 , Ri = $2 \text{ M}\Omega$, Ro = 75Ω , $F_0 \cong 5H_Z$, Supply voltages = \pm 15 V, output voltage swing = \pm 13 V. (a) Determine h-parameter for two port networks. Also draw the hybrid model for **Q.1** 07 CE, CB and CC Configuration. Define Following electrical parameters: input offset voltage, input resistance, **07** CMRR, SVRR, Large signal voltage gain, Output voltage swing, and slew rate. **Q.2** Draw two op-amp based differential amplifier and derive expressions for its gain, 07 input and output resistances, and bandwidth. The 741C op-amp having the following parameters is connected as a non-07 inverting amplifier with $R_1 = 1k\Omega$ and $R_F = 10k\Omega$ compute the values of $A_F, R_{iF}, R_{oF}, f_F, and V_{ooT}$. OR (b) Derive the expression for the closed loop gain, input resistance and output **07** resistance of voltage series feedback amplifier. What is an instrumentation amplifier? Explain with the help of neat diagram the 07 **Q.3** operation of an instrumentation amplifier employing the three basic op-amps and with provision for variation in the voltage gain. Describe the working of an integrator circuit with relevant diagrams. 07 OR Explain voltage to current converter with grounded load. 07 0.3 (a) Draw the circuit op-amp as differentiator and explain with necessary waveforms. **07 (b)** Draw and explain the use of op-amp as a zero crossing detector. 07 **Q.4** (a) **(b)** Explain with circuit diagram the operation of a VCO. 07 Explain the working of a summing and averaging amplifier when connected in 0.4 (a) 07 inverting mode. **07 (b)** Sketch the diagram of 555 timers as an astable multivibrator having 50% duty cycle. Explain its working and derive equation for frequency of output waveform. Explain with the help of circuit diagram, the operation of first order Butterworth **Q.5** (a) 07 low-pass filter. **(b)** Explain op-amp as a comparator. 07 OR**Q.5** What is PLL? Discuss different applications of PLL in detail. 07 (a) Draw and explain basic block schematic of 78×× series three terminal voltage 07

regulator ICs.